

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (E.C.E) II-Semester Main & Backlog Examinations, September-2022

Basic Circuit Analysis

Time: 3 hours

Max. Marks: 60


Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

| Q. No. | Stem of the question | M | L | CO | PO |
|--------|--|---|---|----|----|
| 1. | <p>Determine the unknown voltage or current in the following figures (a) and (b)</p> <p>(a) (b)</p> | 2 | 2 | 1 | 1 |
| 2. | <p>An electroplating apparatus uses electrical current to coat material with metals such as copper or silver. In the figure below, a 220 V electrical DC source supplies 10 A DC to the electroplating apparatus. Then find the cost to operate the apparatus for a single 12 hour day if electric energy costs 10 paisa per kilowatt-hour (kWh)</p> | 2 | 2 | 1 | 1 |
| 3. | <p>Find the compensation voltage that is required when R is changed from 4Ω to 2Ω</p> | 2 | 2 | 2 | 1 |

4. Find I_x using Tellegen's theorem. Assume boxes numbered are circuit elements.

2 3 2 1

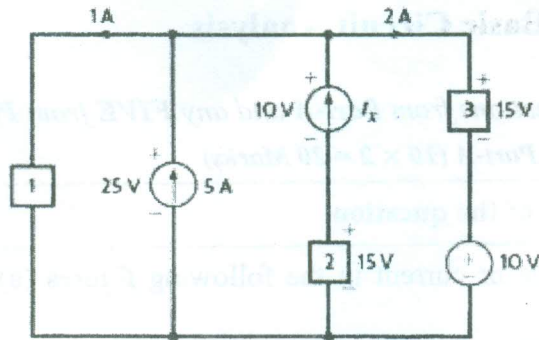


5. What do you mean by Zero input response (ZIR) and Zero state response (ZSR).

2 1 4 1


6. Find the current I_L and the voltage V_C in steady state, for the circuit shown in the figure

2 3 4 2

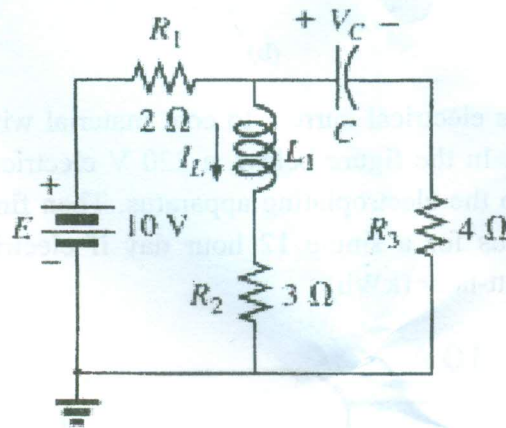

7. Find the quality factor (Q) of the circuit given below.

2 2 3 1

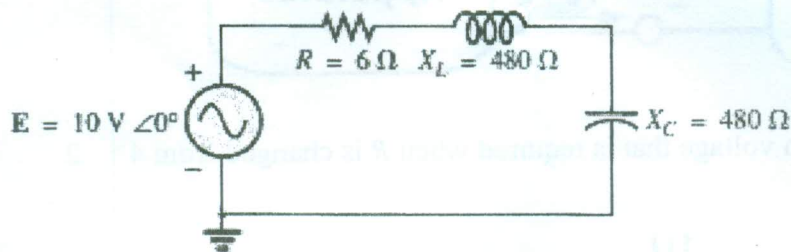

8. Define propagation constant and characteristic impedance of a filter

2 1 5 1

9. Write the condition for symmetry and reciprocity of a two port network in terms of transmission parameters.

2 1 6 1


10. Draw the equivalent circuit of the two-port network in terms of h -parameters.

2 1 6 1

Part-B (5 × 8Marks = 40 Marks)


11. a) Find i_x from the circuit using the mesh analysis

4 2 1 2

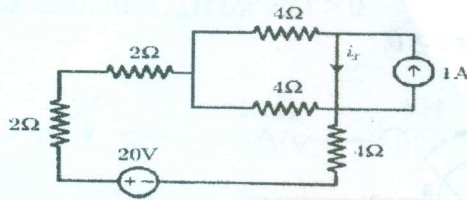


b) Find the voltage across the 5 Ω resistor in the network shown in below figure using the Nodal Analysis.

4 2 1 2

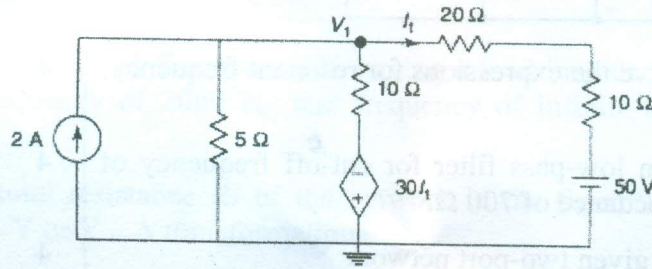


12. a) Two sets of measurements are made on a linear passive resistive network in Fig.(a) and Fig.(b). Find the current through the 2- Ω resistor by using Reciprocity theorem.

4 3 2 3

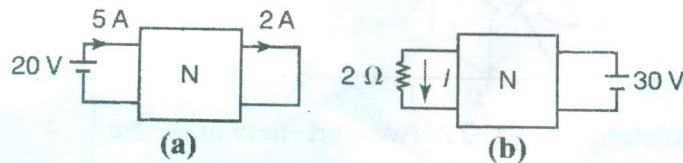

b) Find V_o in the circuit shown below by using Super-position theorem


4 2 2 2

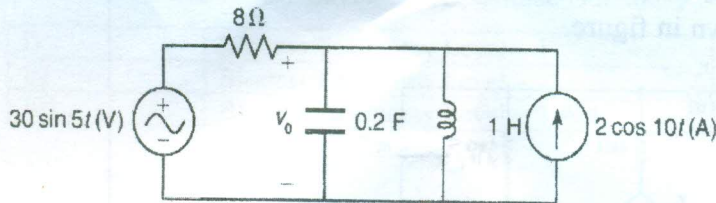

13. a) The switch in the circuit shown in figure below has been in position 'a' for a long time. At $t = 0$, the switch is moved to position 'b'. Then


4 3 4 2

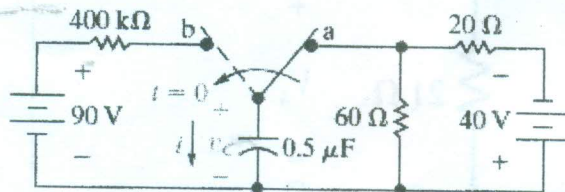- i) Find the expression for $v_C(t)$ when $t \geq 0$
- ii) Determine the time after which voltage across capacitor becomes zero, when switch is in position 'b'.



b) The switch in the circuit shown in figure below has been in position 'a' for a long time. At $t = 0$, the switch moves from position 'a' to position 'b'.

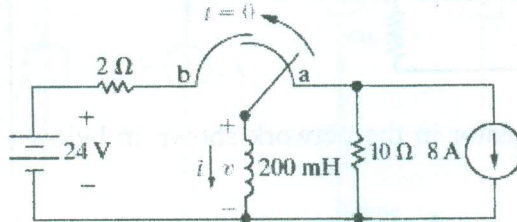- i) Find the expression for $i(t)$ for $t \geq 0$.
- ii) Determine $i(t)$ at $t=0.2$ s.



4 3 4 2

14. a) For a parallel RLC circuit, derive the expressions for resonant frequency, quality factor and bandwidth.


4 1 3 2

b) Design a constant-k, T section low-pass filter for cut-off frequency of 2.5 kHz and nominal load impedance of 700 Ω.

4 4 5 3

15. a) Find the Z – parameters of the given two-port network

4 3 6 2

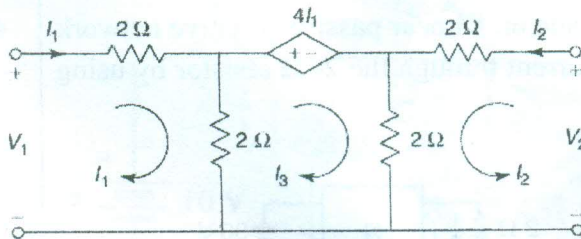


b) Obtain the over-all Y-parameters, when 2 two-port networks are connected parallel.

4 1 6 1


16. a) Determine the value of R_L to deliver maximum power to load and power delivered in the circuit shown in figure.

4 3 2 2

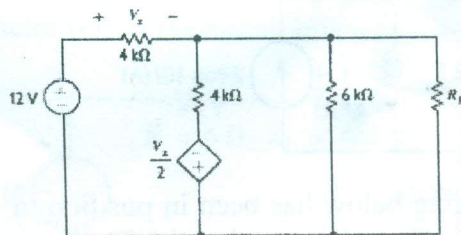

b) Determine the Thévenin and Norton equivalents of the circuit represented in the figure below from the perspective of the open terminals.


4 2 2 2

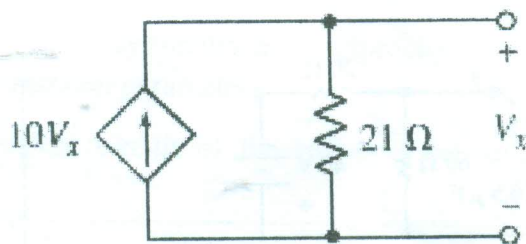

17. Answer any *two* of the following:

- a) The switch is closed at $t = 0$, in the network shown below. Assuming all initial conditions as zero, find $i(t)$ for all $t > 0$

4 2 4 2

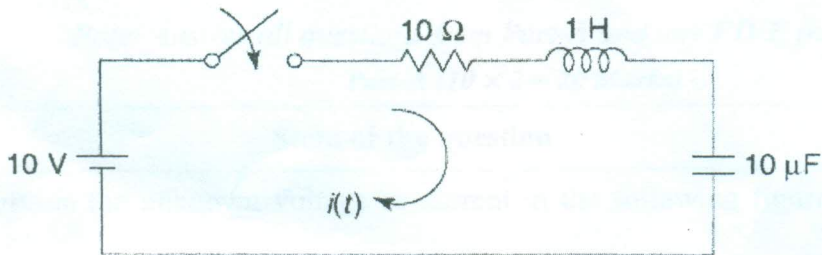


- b) Design a m -derived T-section HPF having a load impedance of 300Ω , cut-off frequency of 2000 Hz and frequency of infinite attenuation is 1700 Hz .

4 4 5 2

- c) Find the total resistance R_T of the network in the figure shown below, using $\Delta - Y$ or $Y - \Delta$ transformations.

4 2 1 2

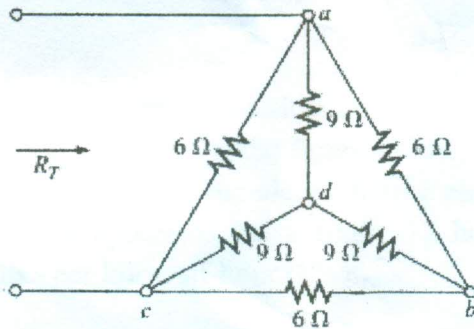

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

| | | |
|------|-------------------------------|-----|
| i) | Blooms Taxonomy Level - 1 | 20% |
| ii) | Blooms Taxonomy Level - 2 | 40% |
| iii) | Blooms Taxonomy Level - 3 & 4 | 40% |
