

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 12315 N

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (E.E.E) II-Semester Main & Backlog Examinations, September-2022

Electrical Measurements and Instrumentation

Time: 3 hours

Max. Marks: 60

Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

Q. No.	Stem of the question	M	L	CO	PO
1.	Discuss briefly accuracy of an instrument.	2	1	1	1,3
2.	Give the classification of instruments.	2	2	1	1,3
3.	Draw the circuit diagram of reactive power measurement by single wattmeter method.	2	3	2	1,2
4.	List the advantages of digital instruments	2	1	2	1,2
5.	Classify the resistance based on the value range.	2	2	3	1,2
6.	Draw the schematic diagram of Wagner's earthing device.	2	3	3	1,2
7.	Draw the circuit diagram for Ammeter calibration using potentiometer.	2	3	4	1,2
8.	Discuss briefly turns ratio of Current Transformer and Potential Transformer.	2	2	4	1,2
9.	List the types of transducers.	2	1	5	1,2
10.	Draw the schematic diagram of bonded strain gauge.	2	3	5	1,2
Part-B (5 × 8 = 40 Marks)					
11. a)	Describe the construction and working of Attraction type moving iron instrument.	5	1	1	1,3
b)	A 1mA meter with an internal resistance of 100Ω is to be converted into a 0-100 mA ammeter, calculate the shunt required.	3	3	1	1,3
12. a)	Explain the measurement of 3-phase power using two-wattmeter method.	5	2	2	1,2
b)	Draw the Lissajous pattern, when the two-input equal sinusoidal voltage signals of same frequency with phase difference 90° are applied to CRO.	3	3	2	1,2

Contd... 2

30

R-107

13. a)	Prove that Kelvin's double bridge doesn't include connecting wire resistance in measurement.	5	4	3	1,2
b)	Explain measurement of Capacitance by Desauty's bridge.	3	2	3	1,2
14. a)	Derive the expression for transformation ratio of a Current Transformer.	5	3	4	1,2
b)	Explain the measurement of resistance by DC Crompton potentiometer.	3	2	4	1,2
15. a)	Explain the measurement of angular velocity using the DC Tachogenerator.	5	2	5	1,2
b)	Explain the measurement of linear displacement using linear Potentiometer.	3	2	5	1,2
16. a)	Prove that the scale of instrument using gravity control is non-uniform.	4	4	1	1,3
b)	Explain the measurement of 3 – phase total reactive power using single wattmeter method.	4	4	2	1,3
17.	Answer any <i>two</i> of the following:				
a)	Deduce the balance equation of general form of an AC bridge.	4	3	3	1,2
b)	Explain the construction of standard resistance with neat sketch.	4	2	4	1,2
c)	Describe about the transducers and their classification.	4	1	5	1,2

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level – 1	20%
ii)	Blooms Taxonomy Level – 2	40%
iii)	Blooms Taxonomy Level – 3 & 4	40%
