

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD*Accredited by NAAC with A++ Grade***B.E. (E.C.E.) III-Semester Supplementary Examinations, August-2022****Digital System Design**

Time: 3 hours

Max. Marks: 60

*Note: Answer all questions from Part-A and any FIVE from Part-B***Part-A (10×2 = 20 Marks)**

Q. No.	Stem of the question	M	L	CO	PO
1.	Draw the logic diagram of binary to Gray code converter.	2	1	1	1
2.	Show that the dual of the Exclusive-OR is equal to its Complement.	2	2	1	2
3.	Explain the need of carry look ahead adders	2	1	2	2
4.	What are the applications of multiplexer and demultiplexer?	2	1	2	1
5.	Define setup and hold times of Flip Flops.	2	1	3	1
6.	Define state diagram and state table.	2	1	3	2
7.	What are the data types in Verilog HDL?	2	1	4	1
8.	Give the syntax of any two system tasks in Verilog HDL.	2	1	4	1
9.	Mention different types of conditional statements used in Verilog HDL.	2	2	5	1
10.	What is meant by logic synthesis?	2	1	5	1
Part-B (5×8 = 40 Marks)					
11. a)	Simplify the Boolean function $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ using Karnaugh map method.	4	3	1	2
b)	State and Prove De Morgan's Laws.	4	2	1	2
12. a)	Explain the operation of BCD adder with a neat circuit and example.	6	2	2	3
b)	Draw the circuit of 4-to-2-line priority encoder with its truth table	2	3	2	2
13. a)	Explain the design and circuit to convert D-Flip Flop to JK Flip Flop.	4	3	3	2
b)	Implement the 4-bit asynchronous up counter using JK Flip Flops.	4	4	3	3
14. a)	Write Verilog HDL code for 4x1 multiplexer in gate level modelling.	4	2	4	2
b)	Write a Verilog HDL code of a full adder in data flow modelling and its test bench.	4	2	4	2
15. a)	Write Verilog code for 1101 sequence detector using Moore FSM	6	4	5	3
b)	Explain the differences between tasks and functions.	2	2	5	2
16. a)	Explain Binary Codes in Detail.	4	4	1	3
b)	Design a 1-bit comparator using gates? Explain the Procedure.	4	3	2	3

17.	Answer any <i>two</i> of the following:				
a)	Implement a pseudo-Random Binary Sequence Generator with shift registers	4	3	3	3
b)	Give the syntax for regular assignment delay and implicit continuous assignment delay in Verilog.	4	2	4	2
c)	Differentiate between Blocking and Non-Blocking assignments.	4	2	5	2

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level - 1	20
ii)	Blooms Taxonomy Level - 2	40
iii)	Blooms Taxonomy Level - 3 & 4	40
