

Hall Ticket Number:

1 6 0 2 2 0 7 3 4 0 5 1

Code No. : 13348 S

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (E.E.E.) III-Semester Supplementary Examinations, August-2022

Electrical Network Analysis


Time: 3 hours

Max. Marks: 60

Note: Answer all questions from **Part-A** and any **FIVE** from **Part-B**

Part-A (10 × 2 = 20 Marks)

Q. No.	Stem of the question	M	L	CO	PO
1.	Define impulse and step input functions.	2	1	1	1
2.	Differentiate transient response and steady state response.	2	1	1	1
3.	Under what conditions, response of RLC series circuit for step input is: i) under damped ii) over damped.	2	1	1	1
4.	Give any two applications of second order circuits.	2	1	1	2
5.	Define quality factor of a resonant circuit.	2	1	2	1
6.	Compare linear transformer and ideal transformer.	2	2	3	2
7.	Give the expressions for symmetry and reciprocal of y and ABCD parameters.	2	1	4	2
8.	A two-port network is defined by the relation: $I_1=5V_1 + 3V_2$, $I_2=2V_1-7V_2$. Calculate the z-parameters.	2	4	4	2
9.	Draw the equivalent circuit of a capacitor in Laplace domain with initial voltage V(0).	2	1	5	2
10.	Define transfer function.	2	1	5	1
Part-B (5 × 8 = 40 Marks)					
11. a)	From the fundamentals, obtain the step response of a series RL circuit.	4	2	1	2
b)	For the circuit shown below, let $V_c(0) = 60$ V. Determine V_c , V_x and i_0 for $t > 0$.	4	4	1	2

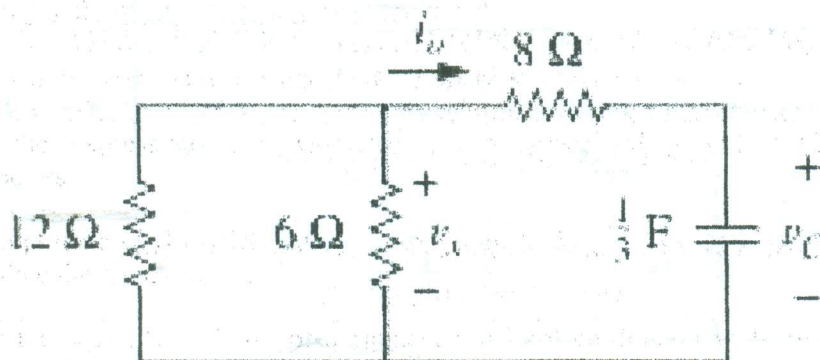


12. a) Derive the expression for circuit current of a series RLC circuit excited by step input.

4 2 1 2

b) In the circuit shown below, find $v(t)$ for $t > 0$.

4 4 1 2

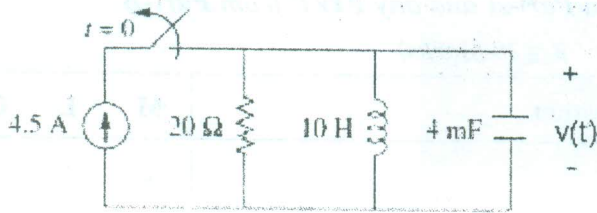


13. a) Derive the expression for half power frequencies of an RLC series circuit.

4 2 2 2


b) Explain the procedure to construct a dual circuit. Also obtain the dual of the circuit shown below.

4 2 3 2

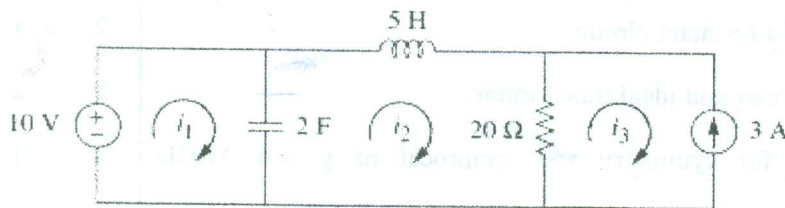


14. a) Consider the series connection of two-port networks shown in Figure below. Show that $[Z] = [Z_a] + [Z_b]$.



4 2 4 2

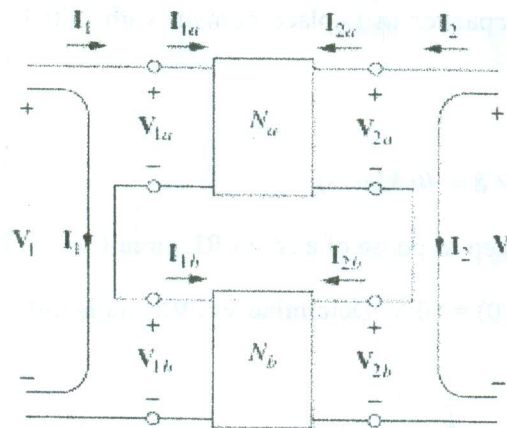

b) Determine the h-parameters for the circuit shown below.

4 4 4 2

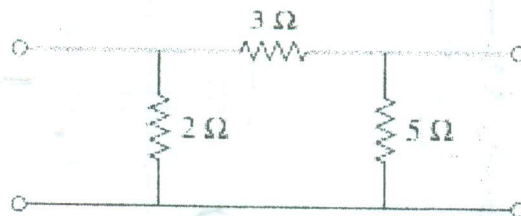

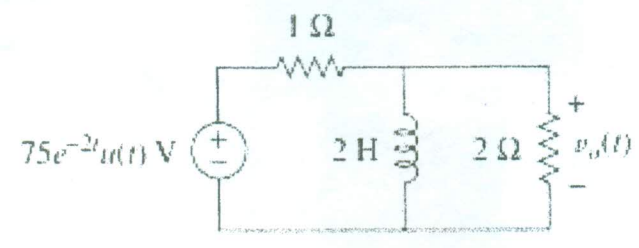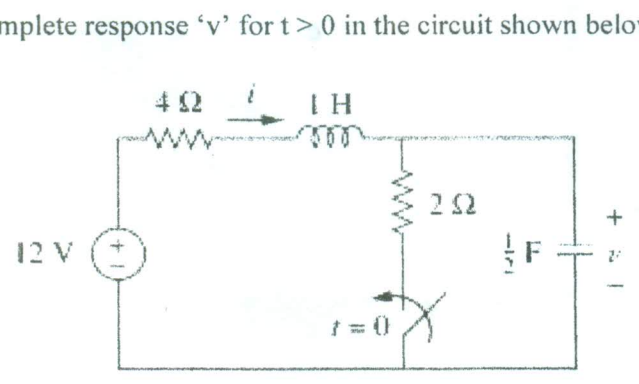15. a)	State and explain convolution theorem.	4	2	5	2
b)	Find $v_0(t)$ for the circuit shown below. Assume zero initial conditions.	4	4	5	2
					
16. a)	A simple RL series circuit is excited by a sinusoidal voltage source. The circuit is initially relaxed. At $t=0$, the switch is closed find the response $i(t)$ for the current. Source voltage is $V_m \cos(\omega t + \phi)$.	4	2	1	2
b)	Find the complete response 'v' for $t > 0$ in the circuit shown below	4	4	1	2
					
17.	Answer any <i>two</i> of the following:				
a)	Derive an expression for energy stored in a coupled circuit.	4	3	3	2
b)	The Z-parameters of a two- port network are $Z_{11}=15 \Omega$, $Z_{12}=Z_{21}=6 \Omega$ and $Z_{22}=24 \Omega$. Determine the ABCD parameters.	4	4	4	2
c)	The output of a linear system is $y(t) = 10 e^{-t} \cos 4t u(t)$ when the input is $x(t) = e^{-t} u(t)$. Find the transfer function of the system and its impulse response.	4	4	5	2

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level - 1	20%
ii)	Blooms Taxonomy Level - 2	37.50%
iii)	Blooms Taxonomy Level - 3 & 4	42.50%
