

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD**

Accredited by NAAC with A++ Grade

**B.E. (E.C.E.) III-Semester Supplementary Examinations, August-2022**





**Network Analysis and Transmission Lines**

Time: 3 hours

Max. Marks: 60

Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

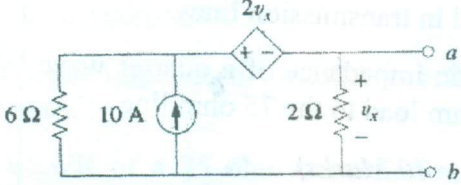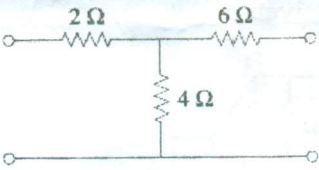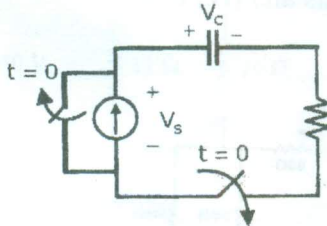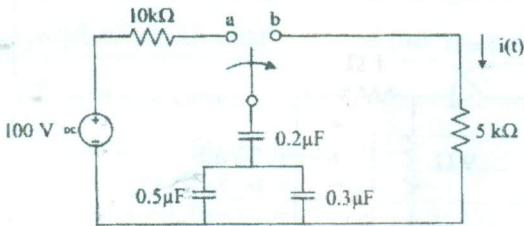Q. No.	Stem of the question	M	L	CO	PO
1.	<p>Find the Norton equivalent circuit of the circuit in figure shown below at terminals a-b.</p> 	2	2	1	2
2.	<p>Find the <math>Y_{12}</math> and <math>Y_{21}</math> parameters for the T network shown in below figure.</p> 	2	1	1	1
3.	<p>A combination of <math>1\mu\text{F}</math> capacitor with an initial voltage <math>V_c(0) = -2\text{V}</math> in series with a <math>100\Omega</math> resistor is connected to a <math>20\text{ mA}</math> ideal dc current source by operating both switches at <math>t = 0\text{s}</math> as shown. Determine the current through resistor at <math>t=0^-</math> and give the justification.</p> 	2	1	2	1
4.	<p>The switch in the circuit shown was on position 'a' for a long time, and is moved to position b at time <math>t = 0</math>. Find the current <math>i(t)</math> for <math>t=0^-</math> and <math>t = \infty</math></p> 	2	2	2	2

5.	What is meant by resonance? Differentiate between series and parallel resonance circuits.	2	2	3	1
6.	Calculate the cut off frequency of a constant K-low pass filter given $L= 50\text{mH}$ and $C= 0.2\mu\text{F}$ .	2	2	4	2
7.	Define wavelength and velocity of propagation in a transmission line	2	1	5	1
8.	Determine the series impedance and shunt admittance of a transmission line characterized by $R=10\Omega/\text{km}$ , $L=0.0037\text{H}/\text{km}$ , $C=0.0083\times 10^{-6}\text{F}/\text{km}$ and $G=0.4\times 10^{-6}\text{S}/\text{km}$ at $1000\text{Hz}$ .	2	1	5	2
9.	Outline the significance of impedance matching and list various impedance matching devices used in transmission lines.	2	2	6	1
10.	What is the value of characteristic impedance of a quarter wave transmission line to match $120\text{ ohm}$ load to the $75\text{ ohm}$ line	2	2	6	2
<b>Part-B (5×8 = 40 Marks)</b>					
11. a)	Define Transmission model parameters and derive the condition for reciprocity of a network	4	1	1	1
b)	Find the h parameters of the network given below.	4	2	1	2
12. a)	Determine both $i_1$ and $i_L$ in the circuit shown in below figure for $t > 0$ and at (i) $t=0^-$ (ii) $t=0^+$ (iii) $t=1\text{ms}$ and (iv) $t=\infty$	4	3	2	3
b)	Find $v(t)$ for $t \geq 0$ . Calculate the initial energy stored in the capacitor.	4	3	2	3



13. a)	A series resonant circuit has $R=2\Omega$ , $L= 1 \text{ mH}$ and $C= 0.3 \mu\text{F}$ , Determine the bandwidth, resonant frequency and quality factor when the input signal of $20 \sin \omega t$ is applied.	4	3	3	2
b)	Design both the T- section and $\pi$ -section m-derived high pass filter with a cut off frequency of 20KHz, design impedance of $400\Omega$ and $m=0.2$ .	4	3	4	3
14. a)	Explain the types of distortions in a transmission line and derive the distortion less condition for transmission.	4	4	5	1
b)	The Characteristic Impedance of a uniform transmission line is $2039.6 \Omega$ at a frequency of 800Hz. At this frequency the propagation constant was found to be $0.054 \angle 87.9^\circ \Omega$ . Determine the values of primary constants.	4	3	5	2
15. a)	Determine the input impedance for $\lambda/2, \lambda/4, \lambda/8$ lines and brief their characteristics.	4	4	5	1
b)	Compute the VSWR of a 75 ohm transmission line when it is terminated by a load impedance of $50+j30$ ohm.	4	3	5	3
16. a)	Find the transmission parameters of the circuit shown below.	4	2	1	2
b)	The switch in the circuit of figure shown below has been closed for a long time. At $t = 0$ , the switch is opened. Calculate $i(t)$ and $V_L$ at $t=1\text{ms}$ .	4	3	2	2
17.	Answer any <i>two</i> of the following:				
a)	Describe the composite filter design and list out the advantages over m-derived filters.	4	1	4	1
b)	Prove that a transmission line of finite length terminated by its characteristic impedance is equivalent to an infinite line.	4	4	5	1
c)	Outline the concept of smith chart and list out its applications.	4	2	6	1

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level – 1	20%
ii)	Blooms Taxonomy Level – 2	30%
iii)	Blooms Taxonomy Level – 3 & 4	50%

\*\*\*\*\*