## Code No.: 17336 S

## VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

## B.E. (E.E.E.) VII-Semester Supplementary Examinations, July-2022

## Switchgear and Protection

Time: 3 hours

Max. Marks: 60

Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A  $(10 \times 2 = 20 \text{ Marks})$ 

Q. No.		Stem	of th	ne qu	estio	n			M	L	CO	PO
1.	Define the following terms with respect to an Over current relay  i) Reset Value ii) Dropout Value							2	1	1	1,2,3,4,12	
2.	Distinguish between an eart	h faul	t and	d phas	e fai	ılt		have been seen as	2	4	1	1,2,3,4,12
3.	Draw the characteristics of	a Mho	rela	y on l	R-X	plane.			2	1	2	1,2,3,4,12
4.	Zone 3 setting of impedance	e relay	at F	R ab is	3		% of 1	ine .	2	4	2	1,2,3,4,12
	R <sub>ab</sub>	bc	و		D	-0-	С	par Branco (100) s par Proper (10) s par (10				
5.	Differential protection disti	nguis	hes l	betwe	en m	nagnet nt of c	izing current	current and fau	lt 2	1	3	1,2,3,4,12
6.	Earthing transformers for	ir	1	pow	er	sys	stem	are use	d 2	1	3	1,2,3,4,12
7.	The factors that affect the are	quen	chin	ig of	arc	in Va	cuum	Circuit Breake	r 2	1	4	1,2,3,4,12
8.	State Recovery rate theory.								2	1	4	1,2,3,4,12
9.	Define the term protective ratio.						2	1	5	1,2,3,4,12		
10.	Illustrate the functions of di	vided	spar	k gap	in n	on line	ear sur	ge diverter.	2	2		1,2,3,4,12
	Pa	rt-B (.	5 × 8	8 = 40	Ma	rks)						
11. a)	Discuss the Classification of the relays based on their time current characteristics.						t 4	1	1	1,2,3,4,12		
b)	The current rating of an overcurrent realy is 5 A. The relay has a plug setting of 150 % and time multiplier setting of 150% and time multiplier setting of 0.4. The CT ratio is 400/5 .Determine the operating time of the relay for a fault current of 6000 A . At TMS=1, operating time at various PSM are given below							t	3	1	1,2,3,4,12	
	PSM	2	4	5	8	10	20	and nitry.				
,	Operating Time in (Sec)	10	5	4	3	2.8	2.4					
12. a)	Explain the working of a m the block diagram.	icro p	roce	ssor b	pased	lover		t relay and draw	v 4	2	2	1,2,3,4,12

Code No.: 17336 S

	b)	For the 66 kV radial feeder shown in figure . Calculate zone 1,2 and 3 setting for the distance relay $R_{ab}$ .	4	3	2	1,2,3,4,12
		A $(4 + j30)$ $R_{bc}$ $(2 + j20)$ $R_{bd}$				Turner in the second
13.	a)	An 11 kV, 100 MVA alternator is provided with differential protection. The percentage of winding to be protected against phase to ground fault is 85%. The relay is set to operate when there is 20% out of balance current. Determine the value of the resistance to be placed in the neutral to ground connection.	4	3	3	1,2,3,4,12
- 3.	b)	What are incipient faults in a transformer and explain how Buchholtz relay can be used to detect the faults.	4	2	3	1,2,3,4,12
14.	a)	In a 132 kV system the inductance and capacitance upto the location of CB are 0.0095 H and 0.015 $\mu F$ respectively. Determine	4	3	4	1,2,3,4,12
		<ul><li>a) The maximum value of restriking voltage across the contacts of CB</li><li>b) Frequency of transient oscillation</li><li>c) The maximum value of RRRV</li></ul>				
	b)	With a neat diagram explain the operation of puffer type SF <sub>6</sub> circuit breaker.	4	2	4	1,2,3,4,12
15.	a)	Discuss the causes of overvoltage in arising on a power system	4	2	5	1,2,3,4,12
	b)	A 33 kV, 3 phase 50 Hz, overhead line 60 km long has a capacitance to ground of each line equal to 0.015 $\mu$ F/kM. determine the inductance and kVA rating of the Peterson coil.	4	3	5	1,2,3,4,12
16.	a)	An earth fault develops at F on the feeder shown in the figure and the fault current is 16000 A. The IDMT relay at point A and B are fed via 800/5 A CTs: The relay at B has a plug setting of 125% and time multiplier setting of 0.2. The circuit breaker take 0.2 seconds to clear the fault and the relay error in each case is 0.15 seconds. For a plug setting of 200 % on the relay A, determine the minimum TMS on that relay for it not to operate before the circuit breaker at B has cleared the fault. The operating time at PSM of 16 for a TMS of 1 is 2.5 Seconds	4	3	1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	1,2,3,4,12
	b)	Discuss the function of each element of control circuit for a three zone step distance relay.	4	2	2	1,2,3,4,12
17.		Answer any <i>two</i> of the following:				par tal
	a)	Draw the schematic of Transformer- Generator unit protection and discuss under what conditions this method will be used.	4	4	3	1,2,3,4,12
	b)	Discuss the process of synthetic testing of circuit breakers for breaking capacity and making capacity of a circuit breaker with the help of a neat circuit diagram.	4	2	4	1,2,3,4,12
	c)	Write a short notes on reducing tower footing resistance.	4	2	5	1,2,3,4,12

M: Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level – 1	23.68%
ii)	Blooms Taxonomy Level – 2	34.22%
iii)	Blooms Taxonomy Level - 3 & 4	42.10%

\*\*\*\*