

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 11124 N/O

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (Civil Engg.) I-Semester Main & Backlog Examinations, Jan./Feb.-2024



Basic Electrical Engineering for Civil Engineers

Time: 3 hours

Max. Marks: 60

Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

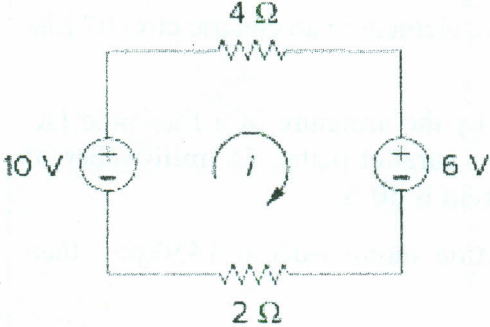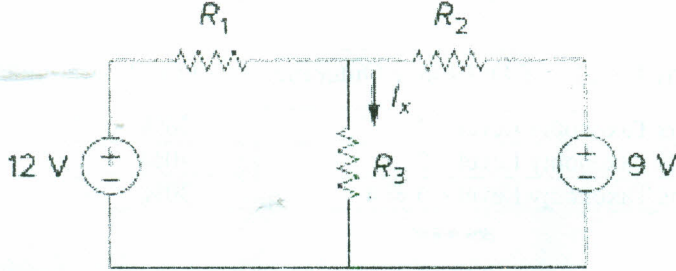Q. No.	Stem of the question	M	L	CO	PO
1.	State the KCL & KVL.	2	1	1	1,2
2.	Give the relation between voltage and current in an inductor	2	1	1	1,2
3.	List the advantages of sinusoidal alternating voltage	2	1	1	1,2
4.	In a three phase balanced Star connected system, if the line voltage is 415V, find the phase voltage.	2	1	1	1,2
5.	Give the classification of DC generators.	2	1	2	1,2
6.	Explain the use of Fleming's Left-Hand rule in DC machine.	2	1	2	1,2
7.	Give the slip of induction motor.	2	1	3	1,2
8.	List the applications of Squirrel Cage three phase induction motor.	2	1	3	1,2
9.	Calculate the current i in the circuit shown, <div style="text-align: center;">  </div>	2	3	1	1,2
10.	An alternating voltage is given by $v = 300\sin 377t$. Determine the peak value and RMS value of the voltage.	2	3	1	1,2
Part-B (5 × 8 = 40 Marks)					
11. a)	Using nodal analysis, determine current I_x in the circuit shown below with $R_1 = 5\ \Omega$, $R_2 = 10\ \Omega$ and $R_3 = 5\ \Omega$. <div style="text-align: center;">  </div>	5	3	1	1,2

b)	Discuss the terms Node, Junction, & Mesh in an electric circuit.	3	2	1	1,2
12. a)	A resistance of $10\ \Omega$ and capacitor of $50\ \mu\text{F}$ are in series and they are connected across 230 V, 50 Hz supply. Calculate (i) impedance of the circuit (ii) current in the circuit.	5	3	1	1,2
b)	Give the advantages of three phase ac supply.	3	2	1	1,2
13. a)	Derive the equation of EMF induced in DC generator.	5	3	2	1,2
b)	Explain the Fleming's Right-Hand rule used in DC machine.	3	2	2	1,2
14. a)	Describe the construction of three phase induction motor with necessary diagram.	5	2	3	1,2
b)	Differentiate between squirrel cage induction motor and slip-ring induction motor.	3	2	3	1,2
15. a)	Using mesh analysis, determine current through $4\ \Omega$ resistor.	5	3	1	1,2
b)	What is an active element & passive element in an electric circuit? List the examples of each element.	3	2	1	1,2
16. a)	Determine the torque established by the armature of a four pole DC motor having 774 conductors, two parallel paths, 24 milli-weber of flux per pole and the armature current is 50 A.	4	3	2	1,2
b)	If a 4-pole 50 Hz 3-phase induction motor runs at 1450rpm, then calculate the value of slip?	4	3	3	1,2
17.	Answer any <i>two</i> of the following:				
a)	Describe the procedure of mesh analysis in electrical circuits with suitable example.	4	2	1	1,2
b)	In series RL circuit, derive the expression for current, impedance, active power consumed and power factor of the circuit.	4	2	1	1,2
c)	Explain the Armature speed control methods of DC shunt motor in detail.	4	2	2	1,2

M : Marks; L: Blooms's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level – 1	20%
ii)	Blooms Taxonomy Level – 2	50%
iii)	Blooms Taxonomy Level – 3 & 4	30%
