

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 11323 N/O

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (E.E.E.) I-Semester Main & Backlog Examinations, Jan./Feb.-2024




Circuit Theory

Time: 3 hours

Max. Marks: 60

Note: Answer all questions from Part-A and any FIVE from Part-B


Part-A (10 × 2 = 20 Marks)

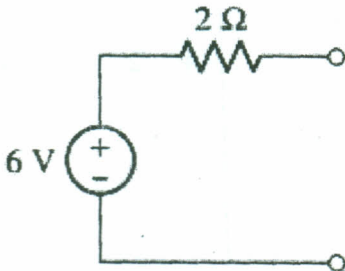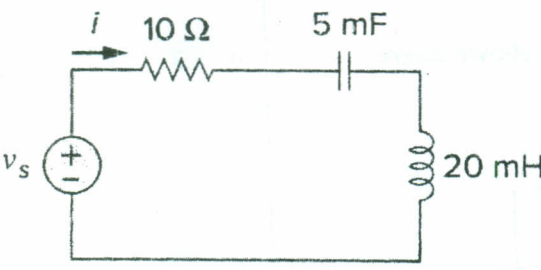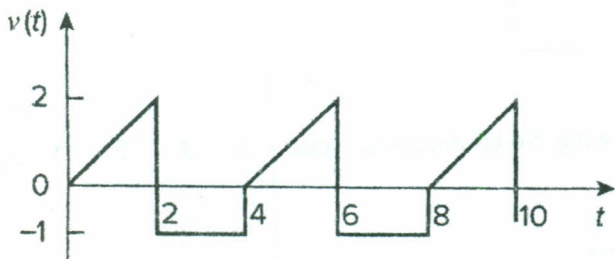Q. No.	Stem of the question	M	L	CO	PO
1.	Define KCL and KVL?	2	1	1	1,2,3,12
2.	Convert the practical voltage source shown below into practical current source? 	2	2	1	1,2,3,12
3.	Represent the network in phasor domain, where $v_s(t) = 115\cos(200t)$ Volts. 	2	2	2	1,2,3,12
4.	Evaluate average value of waveform shown below? 	2	3	2	1,2,3,12
5.	Draw the phasor diagram for the following, when excited by sinusoidal voltage waveform (i) Pure resistive circuit (ii) Pure inductive circuit (iii) Pure capacitive circuit	2	3	3	1,2,3,12
6.	Define power factor of an AC circuit?	2	1	3	1,2,3,12
7.	State Superposition theorem.	2	1	4	1,2,3,12

Contd... 2

8. Calculate the maximum power that can be delivered to the 6Ω resistor, assume source resistance as R_o ?

2 2 4 1,2,3,12

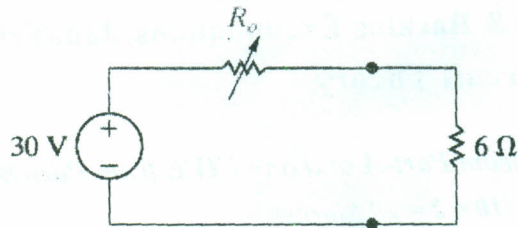

9. Explain the advantages of three phase system?

2 1 5 1,2,3,12

10. Write relation for the following in a delta connected three phase system?


2 2 5 1,2,3,12

- a) Line voltage and phase voltage
- b) Line current and phase current

Part-B (5×8 = 40 Marks)


11. a) Evaluate equivalent resistance (R_{eq}) for the circuit shown below?

4 2 1 1,2,3,12

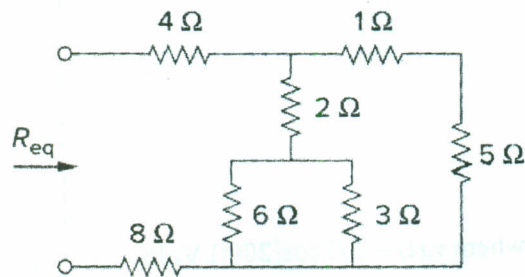


b) Compute the current ' i ' and the value of ' v_o ' in the circuit shown below?

4 2 1 1,2,3,12

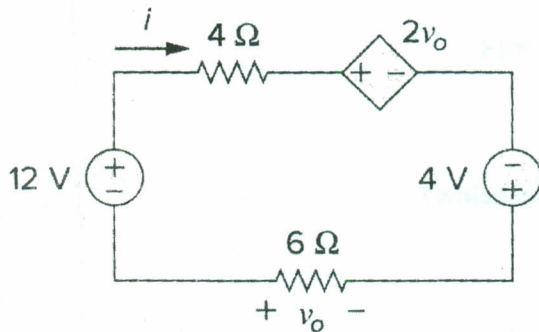


12. a) Find the node voltages in the circuit shown below using Nodal analysis. Node numbers are assigned as 1, 2 and 3 in the circuit.

4 3 2 1,2,3,12

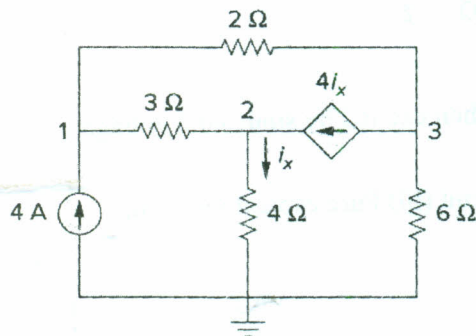

- b) Evaluate the following for the waveform shown below (a) Average value (b) RMS value (c) Form factor (d) Peak factor

4 3 2 1,2,3,12

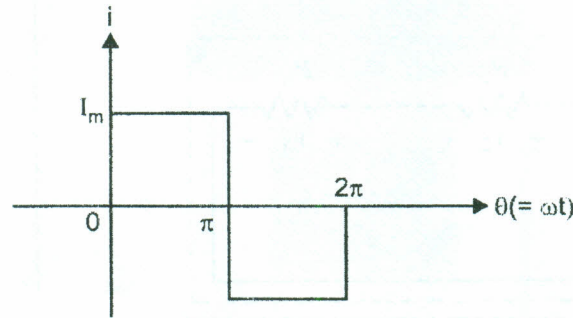

13. a) Show that average power consumed by a pure inductive circuit is zero, when excited by sinusoidal voltage source.


4 2 3 1,2,3,12

- b) A series RLC circuit of resistance R, inductance L and a capacitance C, is excited by an AC voltage source $v = V_m \cos(\omega t)$. Write the expression for the following (a) Inductive reactance and capacitive reactance (b) Impedance of the circuit (c) Current through the circuit (d) Active power consumed by the circuit.

4 1 3 1,2,3,12


14. a) Find Thevenin's equivalent of the circuit shown below across the terminals a-b?

4 3 4 1,2,3,12

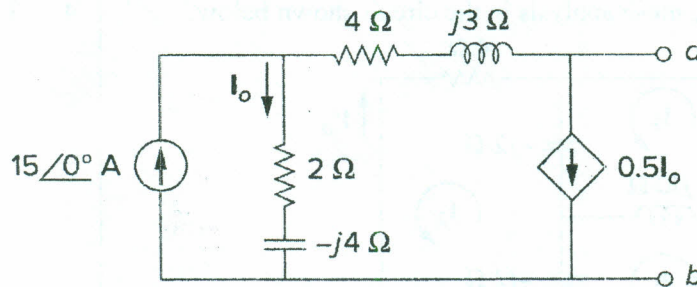

- b) Derive the condition to get maximum power transfer to the load, in an AC excitation circuit of source voltage V_{TH} , source impedance $Z_{TH} = R_{TH} + jX_{TH}$ and load impedance $Z_L = R_L + jX_L$.

4 2 4 1,2,3,12

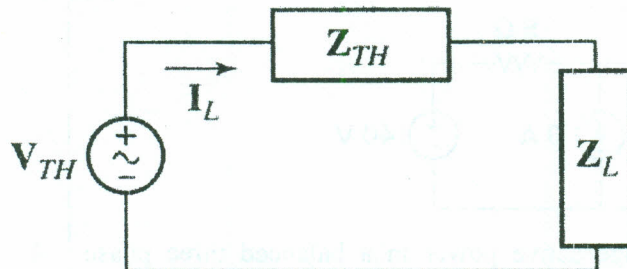


15. a) With a neat diagram, explain the measurement of three phase power using two wattmeter method?

4 2 5 1,2,3,12

- b) A three-phase, balanced delta-connected load of $(4 + j8) \Omega$ is connected across a 415V, 50Hz, three-phase balanced power supply. Determine the phase currents and line currents. Assume phase sequence as RYB.


4 3 5 1,2,3,12

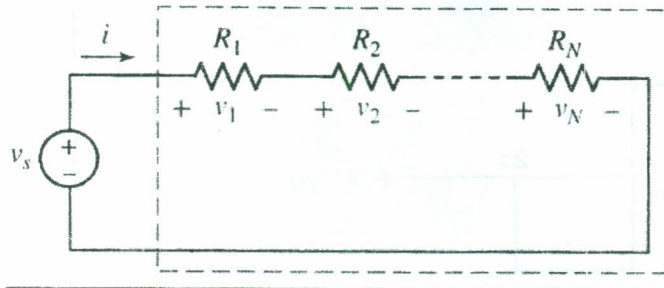16. a) Derive the expression for equivalent resistance of the circuit shown below, if 'N' number of resistors are connected in series across a voltage source V_s . Also derive the expression for voltage across N^{th} resistor?



4 1 1 1,2,3,12

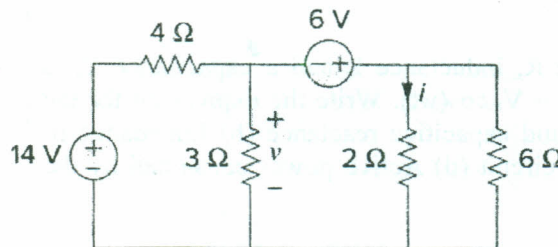
- b) Determine the voltage 'v' and current 'i' in the circuit shown below using Nodal analysis?



4 3 2 1,2,3,12


17. Answer any *two* of the following:

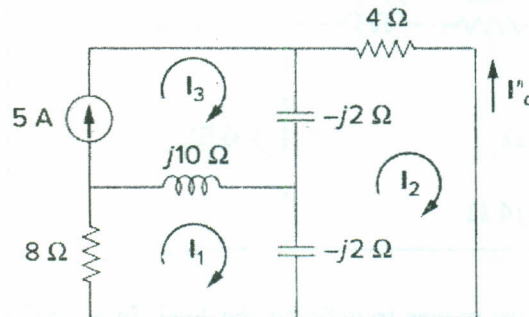- a) Evaluate I_1, I_2, I_3 and I_o'' using mesh analysis in the circuit shown below?



4 3 3 1,2,3,12

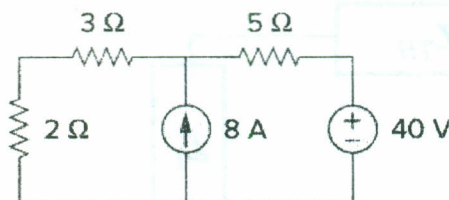- b) Find current through 2Ω resistor in the circuit shown below using Superposition theorem?



4 3 4 1,2,3,12

- c) Derive the expression for average active power in a balanced three phase system?

4 2 5 1,2,3,12

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level – 1	20%
ii)	Blooms Taxonomy Level – 2	40%
iii)	Blooms Taxonomy Level – 3 & 4	40%
