

12. a)	What is meant by time constant? Evaluate the time constant of an RL circuit.	4	2	2	1
b)	For the network shown in Figure, Find the current $i(t)$, when the switch is changed from position 1 to 2 at $t=0$.	4	3	2	2
13. a)	A series resonant circuit has $R=2\Omega$, $L= 1 \text{ mH}$ and $C= 0.3 \mu\text{F}$, Determine the bandwidth, resonant frequency and quality factor when the input signal of $20 \sin \omega t$ is applied.	4	3	3	2
b)	Design a constant K, T- section high pass filter with a cut off frequency of 10KHz, design impedance of 600Ω	4	3	4	2
14. a)	Prove that a transmission line of finite length terminated by its characteristic impedance is equivalent to an infinite line.	4	2	5	4
b)	The Characteristic Impedance of a uniform transmission line is 2039.6Ω at a frequency of 800Hz. At this frequency the propagation constant was found to be $0.054 \angle 87.9^\circ \Omega$. Determine the values of primary constants.	4	3	5	2
15. a)	Estimate the input impedance of $\lambda/2, \lambda/4, \lambda/8$ lines and illustrate their relevance	4	2	6	1
b)	Define Reflection coefficient (Γ) and voltage standing wave ratio (VSWR) and give the minimum and maximum value of reflection coefficient and VSWR	4	2	5	1
16. a)	Explain impedance parameters and admittance parameters of a two port network	4	2	1	1
b)	Differentiate between transient analysis and steady state analysis	4	2	2	1
17.	Answer any <i>two</i> of the following:				
a)	Draw the block diagram of composite filter and explain each block	4	1	4	1
b)	Analyze the reasons for different types of distortions in a transmission line and give the distortion less condition for transmission.	4	4	5	1
c)	Calculate standing wave ratio and reflection coefficient on a line having the characteristic impedance $Z_0= 300 \text{ ohms}$ and the terminating impedance Z_R is $300+j400 \text{ ohms}$	4	3	5	2

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level – 1	20%
ii)	Blooms Taxonomy Level – 2	37.5%
iii)	Blooms Taxonomy Level – 3 & 4	42.5%
