

Hall Ticket Number:

1 6 0 2 2 2 9 2 4 0 2 8

Code No. : 13366 N/O

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (E.E.E.) III-Semester Main & Backlog Examinations, Jan./Feb.-2024**Electrical Network Analysis**

Time: 3 hours

Max. Marks: 60

Note: Answer all questions from **Part-A** and any **FIVE** from **Part-B****Part-A (10 × 2 = 20 Marks)**

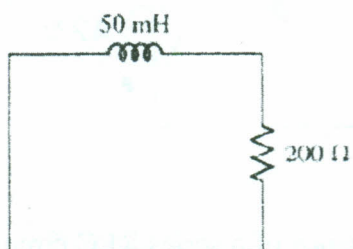
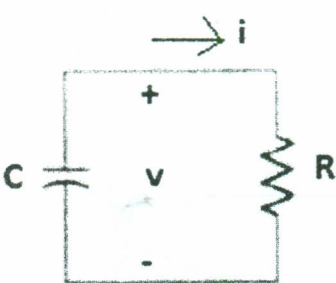
Q. No.	Stem of the question	M	L	CO	PO
1.	Distinguish between transient state response and steady state response.	2	1	1	1,2
2.	Determine the time constant of the network shown in figure. <div style="text-align: center;">  </div>	2	2	1	1,2
3.	Draw the step response of source free RLC series network.	2	1	2	1,2
4.	Give a practical example for a second order system.	2	2	2	1,2
5.	What are the properties of ideal transformer?	2	1	3	1,2
6.	For a series RLC Circuit $R=2\Omega$, $L=1\text{mH}$ and $C=0.4\ \mu\text{F}$, Determine the Band width of the circuit.	2	2	3	1,2
7.	Write the condition for reciprocity of a two port network in terms of A,B,C and D Parameters.	2	1	4	1,2
8.	For a two port network admittance matrix is given by $\begin{bmatrix} 1 & 3 \\ 4 & 1 \end{bmatrix}$. Determine the value of Z_{22} .	2	2	4	1,2
9.	Define zero of a transfer function.	2	1	5	1,2
10.	State initial theorem and final value theorem.	2	1	5	1,2
Part-B (5 × 8 = 40 Marks)					
11. a)	For the source free RC network shown in figure 1, derive the voltage across capacitor $v(t)$ for $t > 0$. Assume that the initial voltage across capacitor is $v(0) = V_0$. <div style="text-align: center;">  </div>	4	2	1	1,2

Figure 1

- b) Define singularity functions and give examples. 4 1 1 1,2
12. a) Classify the response across capacitor of series RLC circuit based on the roots of characteristic equation. 4 2 2 1,2
- b) For the circuit shown in figure 2, the switch is open for a long time but closed at $t=0$. Determine a) $i(0^+)$ b) $v(0^+)$ c) $di(0^+)/dt$ and $dv(0^+)/dt$ 4 3 2 1,2

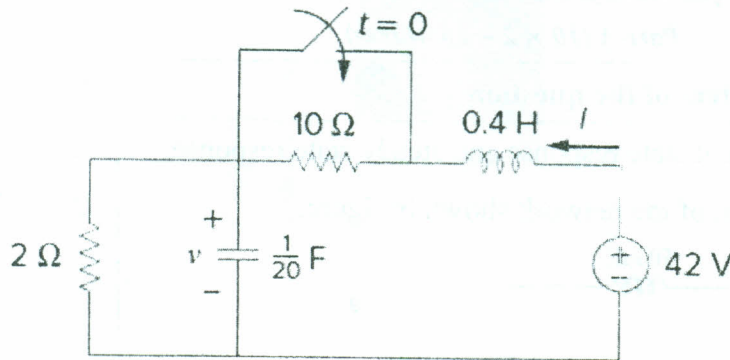


Figure 2

13. a) Derive the expression for resonant frequency of a series RLC circuit and prove that resonant frequency ω_0 is the geometric mean of two half power frequencies ω_1 and ω_2 . 4 2 3 1,2
- b) Calculate the phasor currents I_1 and I_2 in the circuit shown in Figure 3. 4 3 3 1,2

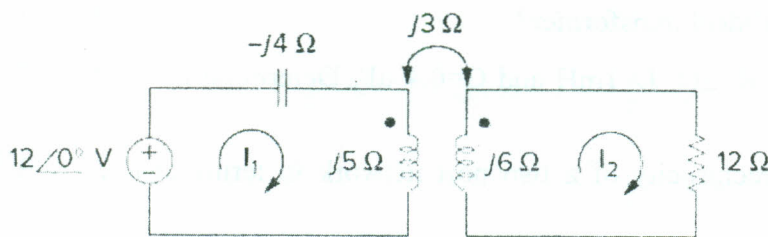


Figure 3

14. a) Prove that Impedance parameters of a two port network, formed by the series connection of two two-port networks is the sum of the z parameters for the individual networks. 4 2 4 1,2
- b) Find the transmission parameters for the two-port network shown in Figure 4. 4 3 4 1,2

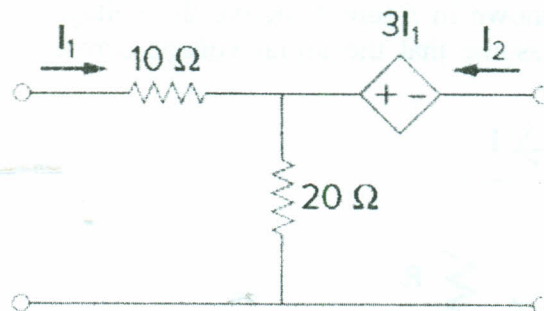


Figure 4

15. a)	State and explain convolution theorem.	4	2	5	1,2
b)	Apply Laplace's transform technique to determine the value of the voltage across the capacitor shown in figure 5 assuming that the value of $v_s(t) = 10u(t)$ V and assume that at $t = 0$, -1 A flows through the inductor and $+5$ V is across the capacitor.	4	3	5	1,2
Figure 5					
16. a)	Explain the complete response of a series RL network subjected to Step response.	4	2	1	1,2
b)	For a source free parallel RLC circuit, assuming that initial voltage across capacitor is $v(0) = 5$ V, initial current through the inductor $i(0) = 0$, $L = 1$ H, $C = 10$ mF and $R = 6.25$ Ω . Find $v(t)$ (voltage across capacitor) for $t > 0$.	4	3	2	1,2
17.	Answer any <i>two</i> of the following:				
a)	Define Duality and write at least four dual pairs of Electrical Networks.	4	1	3	1,2
b)	Find the y parameters of the two-port network shown in Figure 6.	4	3	4	1,2
Figure 6					
c)	Write and explain any four properties of Laplace's Transforms.	4	2	5	1,2

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level – 1	23.75%
ii)	Blooms Taxonomy Level – 2	33.75%
iii)	Blooms Taxonomy Level – 3 & 4	42.5%
