

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 13364 N/O

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (E.E.E.) III-Semester Main & Backlog Examinations, Jan./Feb.-2024**Electronics Engineering-I**

Time: 3 hours

Max. Marks: 60

Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

Q. No.	Stem of the question	M	L	CO	PO	PSO
1.	Define the following terms related to Rectifiers: a) Peak Inverse Voltage b) % Efficiency	2	1	2	1	2
2.	A Silicon diode has a reverse saturation current of 10.5 μA at room temperature of 27°C. Determine reverse saturation current at 60°C.	2	3	1	2	2
3.	Define α , β and γ of a transistor. find the relation between them.	2	1	1	1	2
4.	What is early effect and briefly explain the same.	2	1	1	1	2
5.	State Miller's theorem and mention it's importance in the analysis of amplifier.	2	1	4	1	2
6.	Draw the Common Base Hybrid model, indicate each component and write it's importance.	2	1	4	1	2
7.	What is threshold voltage in Metal Oxide Semiconductor Field Effect Transistor and write it's importance.	2	1	1	1	2
8.	An N channel JFET has $I_{DSS}=10\text{mA}$ and $V_p=-6\text{V}$. Determine the I_D for $V_{gs}=-2\text{V}$ in the pinch-off region.	2	3	1	2	2
9.	Mention the procedure how amplitude can be measured using a CRO.	2	1	3	1	2
10.	Write the working principle of Light Emitting Diode and write the applications of LED.	2	1	3	1	2
Part-B (5 × 8 = 40 Marks)						
11. a)	Explain the working of PN junction diode under forward bias and Reverse bias conditions with the necessary diagrams.	4	2	1	1	2
b)	A full-wave rectifier uses two diodes, the internal resistance of each diode may be assumed constant at 20 Ω . The transformer r.m.s secondary voltage from centre tap to each end of secondary is 50 V and load resistance is 980 Ω . Find i) Max a.c voltage, V_m ii) Max. load current, I_m iii) Average load current, V_{dc} iv) the r.m.s value of load current.	4	3	2	2	2
12. a)	Explain the input and output characteristics of Common Emitter Configuration with relevant diagrams.	4	2	1	1	2
b)	Draw the Collector to base bias circuit and find the expression for stability factor.	4	3	1	2	2
13. a)	Derive the generalized expression for the following of amplifier constructed using Bipolar junction transistor i) Current Gain ii) Voltage gain.	5	3	4	2	2

Contd... 2

b)	When simplified h-model will be used for analyzing BJT amplifier and how it is derived from exact model.	3	3	4	2	2
14. a)	Explain the operation of N-Channel E-MOSFET and obtain it's VI-Characteristics.	4	2	1	2	2
b)	Obtain the Voltage gain and input impedance of the JFET constructed as Common Source amplifier.	4	3	5	2	2
15. a)	Draw the block diagram of CRO and explain the functionality of each block.	5	2	3	1	2
b)	Explain the operation of Photo Diode with neat sketches.	3	2	3	1	2
16. a)	Explain the operation of Zener as voltage regulator with required diagrams.	4	2	1	1	2
b)	In a Silicon transistor circuit with a fixed bias, $V_{CC}=9V$, $R_C=3K\Omega$, $R_B=8K\Omega$, $\beta = 50$, $V_{BE}=0.7V$. Find the operating point and Stability factor.	4	3	1	2	2
17.	Answer any <i>two</i> of the following:					
a)	A Common collector as shown below. The h-parameter are $h_{ie}=1.1k\Omega$, $h_{re}=4 \times 10^{-4}$, $h_{fe}=86$ and $h_{oe}=2\mu A/V$. Compute the Current gain A_i , the Input impedance Z_i .	4	4	4	2	2
b)	With a neat constructional diagram, explain the working of N-channel JFET.	4	2	1	1	2
c)	Explain the operation of UJT and show the negative resistance region.	4	2	3	2	2

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level – 1	20%
ii)	Blooms Taxonomy Level – 2	40%
iii)	Blooms Taxonomy Level – 3 & 4	40%
