

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 11113 S N/O

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (Civil Engg.) I-Semester Supplementary Examinations, August-2023

Basic Electrical Engineering for Civil Engineers


Time: 3 hours

Max. Marks: 60

Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

Q. No.	Stem of the question	M	L	CO	PO
1.	Define Kirchoff voltage law.	2	1	1	1,2
2.	Write the relation between voltage and current in a capacitor.	2	1	1	1,2
3.	An alternating voltage is given by $v = 50\sin 314t$. Determine the form factor of the voltage.	2	2	1	1,2
4.	Give any two advantages of three phase ac supply.	2	1	1	1,2
5.	Explain the use of Fleming's Left Hand rule in a DC machine.	2	1	2	1,2
6.	Write the equation of torque produced by armature in DC motor.	2	1	2	1,2
7.	If a 4-pole 50 Hz 3-phase induction motor runs at 1400 rpm, then calculate the value of slip?	2	2	3	1,2
8.	List any two applications of three phase induction motor.	2	1	3	1,2
9.	Write the statements of Kirchoff current law.	2	1	1	1,2
10.	Describe the significance of power factor in AC electrical circuits.	2	1	1	1,2
Part-B (5 × 8 = 40 Marks)					
11. a)	What is a passive element in an electric circuit? And why resistor is an example of a passive element?	4	2	1	1,2
b)	Using mesh analysis, determine current I_x in the circuit shown below with $R_1 = 6 \Omega$, $R_2 = 12 \Omega$ and $R_3 = 8 \Omega$.	4	3	1	1,2

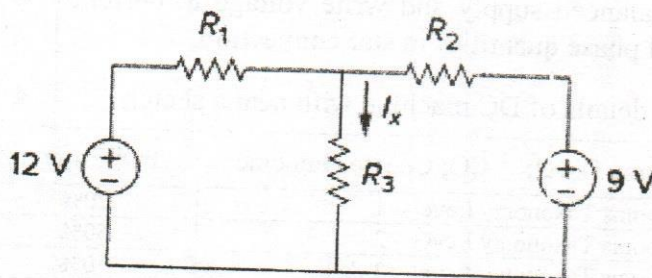

12. a)	In series RL circuit, derive the expression for current, impedance, active power consumed and power factor of the circuit.	4	2	1	1,2
b)	A resistance of $30\ \Omega$ and inductor of $79.5\ \mu\text{F}$ are in series and they are connected across $100\ \text{V}$, $50\ \text{Hz}$ supply. Calculate (i) current in the circuit, (ii) impedance of the circuit and (iii) power consumed and (iv) power factor of the circuit.	4	3	1	1,2
13. a)	Write the terminal voltage equations for different types of DC motors.	4	2	2	1,2
b)	Determine the torque established by the armature of a six pole wave wound DC motor having 920 conductors, $18\ \text{mWb}$ and the armature current is $30\ \text{A}$.	4	3	2	1,2
14. a)	Describe the construction of three phase induction motor with a neat schematic diagram.	4	2	3	1,2
b)	Explain the principle of three phase induction motor with a neat diagram.	4	2	3	1,2
15. a)	Describe the procedure of nodal analysis in electrical circuits with suitable example.	4	2	1	1,2
b)	In series RC circuit, derive the expression for current, impedance, active power consumed and power factor of the circuit.	4	3	1	1,2
16. a)	Explain the speed control methods of DC shunt motor in detail.	4	2	2	1,2
b)	Explain the production of rotating magnetic field in three phase induction motor	4	3	3	1,2
17.	Answer any <i>two</i> of the following:				
a)	Using mesh analysis, determine current through $4\ \Omega$ resistor.	4	3	1	1,2
b)	What is a three phase balanced supply and write voltage & current relation between line and phase quantities in star connection.	4	2	1	1,2
c)	Explain the construction details of DC machine with neat a sketch.	4	2	2	1,2

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level - 1	20%
ii)	Blooms Taxonomy Level - 2	50%
iii)	Blooms Taxonomy Level - 3 & 4	30%
