

Hall Ticket Number:

1 6 0 2 2 2 9 3 5 1 1 3

Code No. : 12426 AS N/O

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (E.C.E.) II-Semester Advanced Supplementary Examinations, September-2023



Basic Circuit Analysis

Time: 3 hours


Max. Marks: 60

Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

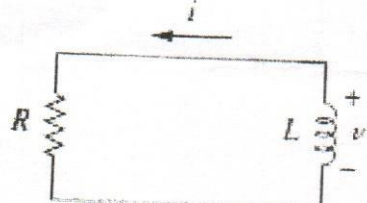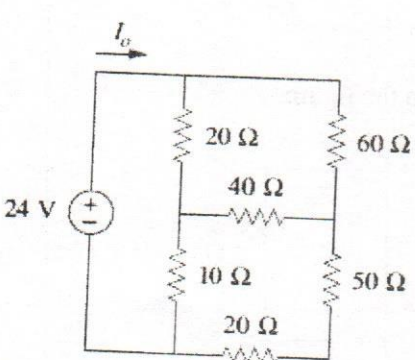
Q. No.	Stem of the question	M	L	CO	PO	PSO
1.	Draw the circuits of dependent voltage and current sources.	2	1	1	1	1
2.	A stove element draws 15 A, when connected to a 240-V line. Determine the time it takes to consume 180 kJ.	2	1	1	2	1
3.	State compensation theorem. Mention its applications.	2	1	2	1	1
4.	Define Kirchoff's current and voltage laws.	2	1	2	1	1
5.	The ABCD parameters of a reciprocal two port network are given as $A=1$ , $B=2$ and $C=3$ . Calculate the $D$ parameter.	2	1	3	1	1
6.	Determine the $h_{12}$ parameter from the given two port network equations: $V_1 = 5I_1 + 2I_2$ , $V_2 = 2I_1 + I_2$	2	2	3	2	1
7.	Define zero input and zero state response.	2	1	4	1	1
8.	For the circuit shown in Figure, $v = 100$ V and $i = 25$ A. Find the value of $L$ and $R$ .	2	2	4	2	1
						
9.	Define quality factor of a resonant circuit. Write its significance.	2	1	5	1	1
10.	What are passive filters? Write classification of filters.	2	1	5	2	1
<p><b>Part-B (5 × 8 = 40 Marks)</b></p>						
11. a)	Calculate $I_o$ in the circuit shown in below figure, using network reduction techniques.	4	2	1	3	1
						

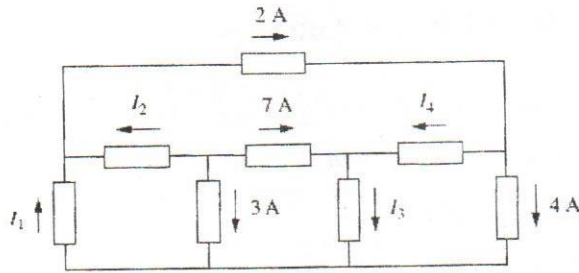b) For the circuit shown in figure, use KCL to find the branch currents  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_4$ .



4 2 1 2 1

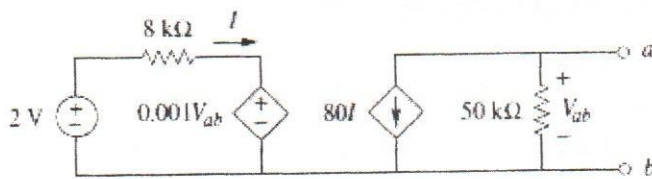
12. a) Determine the Thevenin's equivalent at terminals  $a-b$  of the circuit shown in figure:



4 2 2 3 1

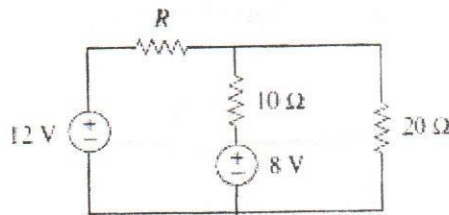
b) Compute the value of  $R$  that results in maximum power transfer to the  $10\Omega$  resistor shown in figure.

Find the maximum power delivered to  $10\Omega$  resistor.




4 3 2 4 1

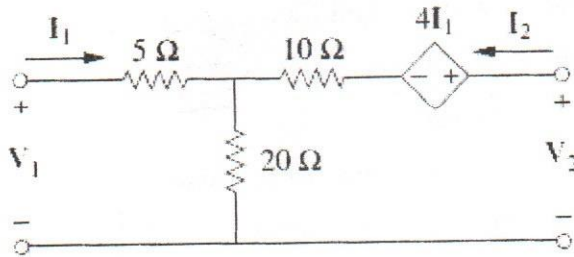13. a) Compute the  $z$ - parameters of the circuit shown in figure.




4 3 3 3 1

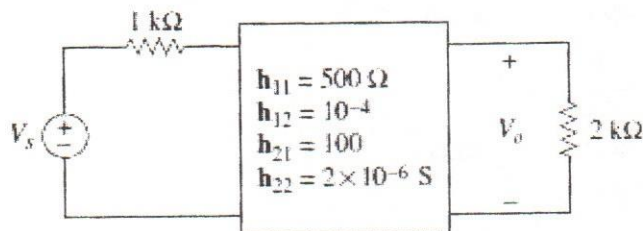b) Determine  $V_o/V_s$  for the network shown in the figure,




4 3 3 4 1

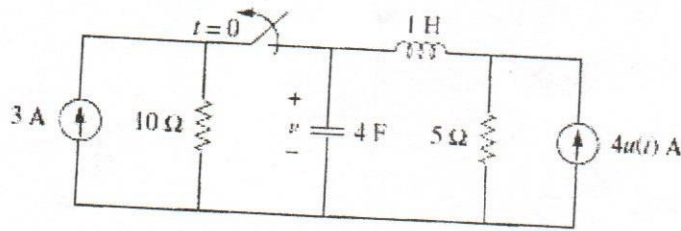14. a) The switch is opened instantaneously at  $t=0$ . Find  $v(t)$  for  $t > 0$  in the circuit shown in figure



4 3 4 3 1

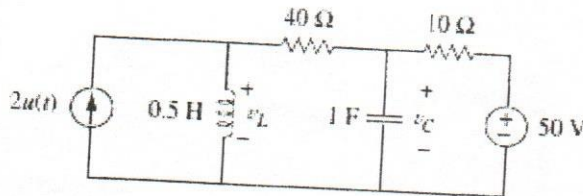- b) Consider the circuit shown in figure, Find  $V_L(0^+)$ ,  $V_C(0^+)$ ,  $V_L(\infty)$  and  $V_C(\infty)$ .



4 2 4 3 1


15. a) Prove that RC low pass filter will act as Integrator.

4 3 5 4 1

- b) A parallel resonant circuit has  $R=100K\Omega$ ,  $L=20mH$  and  $C=5nF$ . Calculate  $\omega_0$ ,  $\omega_L$ ,  $\omega_H$ ,  $Q$ , and  $B$ .

4 2 5 3 1

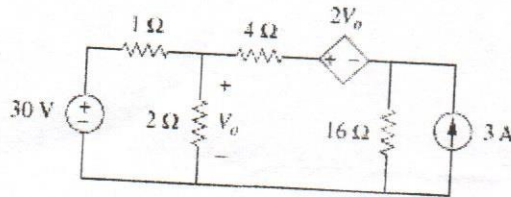16. a) Find  $V_O$  in the circuit shown in figure, using nodal analysis



4 2 1 4 1

- b) State and prove reciprocity theorem with an example.

4 3 2 3 1


17. Answer any two of the following:

- a) Prove that z- parameters for the overall network are the sum of the z- parameters for the individual networks, when connected in series.

4 3 3 3 1

- b) Find  $I_1$  and  $I_2$  in the circuit shown in figure, using Mesh analysis.

4 2 4 4 1

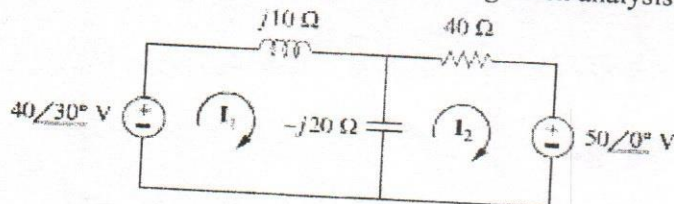

- c) Draw the step response of RC high pass filter and derive the expression for output voltage.

4 3 5 2 1

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level - 1	20%
ii)	Blooms Taxonomy Level - 2	40%
iii)	Blooms Taxonomy Level - 3 & 4	40%