

Hall Ticket Number:

|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

Code No. : 12225 N/O

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. II-Semester Main &amp; Backlog Examinations, August-2023

Basic Electrical Engineering

(Common to N : CSE, AIML &amp; ECE O : Civil, Mech. &amp; IT)

Time: 3 hours

Max. Marks: 60

Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

| Q. No. | Stem of the question   | M | L | CO | PO       |
|--------|--|---|---|----|----------|
| 1.     | Compute $R_{eq}$ for the circuit shown below?<br>  | 2 | 3 | 1  | 1,2,3,12 |
| 2.     | Define KCL and KVL?  | 2 | 1 | 1  | 1,2,3,12 |
| 3.     | Explain the significance of RMS value of a sinusoidal waveform?  | 2 | 2 | 2  | 1,2,3,12 |
| 4.     | Draw the phasor diagram of series R-L-C circuit, when Capacitive reactance( $X_C$ ) is greater than inductive reactance( $X_L$ )?  | 2 | 2 | 2  | 1,2,3,12 |
| 5.     | With neat sketch, describe different types of DC generators based on excitation?   | 2 | 1 | 3  | 1,2,3,12 |
| 6.     | A DC motor takes an armature current of 110A at 480 V. The armature circuit resistance is $0.2\Omega$ . The machine has 6-poles and the armature is lap-connected with 864 conductors. The flux per pole is 0.05 Wb. Calculate the gross torque developed by the armature? | 2 | 3 | 3  | 1,2,3,12 |
| 7.     | Illustrate the comparison of Fuse and MCB?   | 2 | 1 | 4  | 1,2,3,12 |
| 8.     | Evaluate the electrical energy consumed in kWh when operating ten 50W bulbs for 10hours in a day for one month (30days)?   | 2 | 1 | 4  | 1,2,3,12 |
| 9.     | List out any four applications of stepper motor?   | 2 | 2 | 5  | 1,2,3,12 |
| 10.    | Draw the torque-slip characteristics of a three-phase induction motor? Identify the region of stable operation and justify the same?   | 2 | 2 | 5  | 1,2,3,12 |

Contd... 2

|   |   | <b>Part-B (5×8 = 40 Marks)</b> |   |   |          |
|---|---|--------------------------------|---|---|----------|
| 11. a)  | Calculate $V_o$ of the circuit shown below using Nodal analysis?  | 4                              | 3 | 1 | 1,2,3,12 |
|   |   |                                |   |   |          |
| b)  | State the maximum power transfer theorem. Derive the condition for the maximum power transfer to the load in a circuit?   | 4                              | 2 | 1 | 1,2,3,12 |
| 12. a)  | Evaluate the following for the sinusoidal waveform?   | 4                              | 2 | 2 | 1,2,3,12 |
| <ul style="list-style-type: none"> <li>i) RMS value</li> <li>ii) Average value</li> <li>iii) Form factor</li> <li>iv) Peak factor</li> </ul>  |   |                                |   |   |          |
| b)  | For the circuit shown below, determine the following?   | 4                              | 3 | 2 | 1,2,3,12 |
| <ul style="list-style-type: none"> <li>i) Impedance</li> <li>ii) Power factor</li> <li>iii) Instantaneous value of current in the circuit</li> <li>iv) Active power supplied by the source</li> </ul> |   |                                |   |   |          |
|   |   |                                |   |   |          |
| 13. a)  | Derive the emf equation in DC generator?  | 4                              | 2 | 3 | 1,2,3,12 |
| b)  | A 230V DC shunt motor has an armature resistance of $0.5 \Omega$ and field resistance of $115 \Omega$ . At no load, the speed is 1200r.p.m. and the armature current 2.5A. On application of rated load, the speed drops to 1120r.p.m. Determine the following, when the motor delivers rated load? | 4                              | 3 | 3 | 1,2,3,12 |
| <ul style="list-style-type: none"> <li>i) Field current</li> <li>ii) Armature current</li> <li>iii) Line current and</li> <li>iv) Power input to the motor</li> </ul>                                 |   |                                |   |   |          |



|        |  |   |   |   |          |
|--------|--|---|---|---|----------|
| 14. a) | Explain the working principle of a transformer? Draw the phasor diagram of a practical transformer with lagging power factor load?   | 4 | 2 | 4 | 1,2,3,12 |
| b)     | A 20 kVA, 2000V/200 V, single phase, 50 Hz transformer has a primary resistance of $2.5\Omega$ and reactance of $4.8\Omega$ . The secondary resistance and reactance are $0.01\Omega$ and $0.018\Omega$ respectively. The no-load current drawn by the transformer is 0.3A at a power factor of 0.25 lagging, when high-voltage(HV) side is primary, evaluate the following?<br>i) Equivalent resistance and reactance referred to primary<br>ii) Equivalent resistance and reactance referred to secondary<br>iii) Magnetizing current drawn by the transformer<br>iv) Iron losses of the transformer | 4 | 3 | 4 | 1,2,3,12 |
| 15. a) | Explain about rotating magnetic field theory in a 3-phase induction motor?   | 4 | 2 | 5 | 1,2,3,12 |
| b)     | Explain the working of Brushless DC (BLDC) motor with a neat sketch?   | 4 | 1 | 5 | 1,2,3,12 |
| 16. a) | For the figure shown below, evaluate $I_1$ using Superposition theorem?  | 4 | 3 | 1 | 1,2,3,12 |
|        |  |   |   |   |          |
| b)     | Three similar coils each having a resistance of $5\Omega$ and an inductance of $0.02H$ are connected in star to a $440V$ , 3-phase, 50Hz supply. Calculate the phase current, line current, phase voltage and line voltage of the system?  | 4 | 3 | 2 | 1,2,3,12 |
| 17.    | Answer any <i>two</i> of the following:  |   |   |   |          |
| a)     | Illustrate various speed control techniques in DC Shunt motor?   | 4 | 2 | 3 | 1,2,3,12 |
| b)     | Define power factor? Explain static capacitor method of power factor improvement in a series R-L load circuit with phasor diagram?   | 4 | 3 | 4 | 1,2,3,12 |
| c)     | Explain the construction and working of variable reluctance Stepper motor?   | 4 | 1 | 5 | 1,2,3,12 |

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

|      |                               |     |
|------|-------------------------------|-----|
| i)   | Blooms Taxonomy Level - 1     | 20% |
| ii)  | Blooms Taxonomy Level - 2     | 40% |
| iii) | Blooms Taxonomy Level - 3 & 4 | 40% |

\*\*\*\*\*