

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 12323 O

**VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD**

Accredited by NAAC with A++ Grade

**B.E. (E.E.E.) II-Semester Backlog Examinations, August-2023**

**Circuit Theory**

Time: 3 hours

Max. Marks: 60


Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)


Q. No.	Stem of the question	M	L	CO	PO
1.	What are the differences between dependent and independent sources?	2	1	1	1,2
2.	State the source Transformation principle.	2	1	1	1,2
3.	Define phase angle and phase difference.	2	1	2	1,2
4.	Define peak factor of an alternating quantity.	2	1	2	1,2
5.	The resistance of a coil is $140 \Omega$ and its inductance is $0.85 \text{ H}$ . Find the current, the power factor and the circuit impedance when the coil is connected to $120 \text{ V}$ , $60 \text{ Hz}$ supply.	2	3	3	1,2,3
6.	Draw the impedance triangle of series R-L and R-C circuits.	2	1	3	1,2
7.	State the maximum power transfer theorem.	2	1	4	1,2
8.	What is the condition for the maximum power to be transferred in AC circuit?	2	1	4	1,2
9.	A three-phase, three-wire balanced delta -connected load yields wattmeter readings of $1154 \text{ W}$ and $557 \text{ W}$ . Find the power factor of the load.	2	4	5	1,2,3
10.	What do you understand by a balanced load of a three phase circuit?	2	1	5	1,2
<b>Part-B (5 × 8 = 40 Marks)</b>					
11. a)	Using source transformation, calculate power dissipated in $10\Omega$ resistor in the circuit shown in figure:	4	4	1	1,2,3
b)	State and explain Kirchoff's current law and voltage law with examples.	4	2	1	1,2

Contd... 2

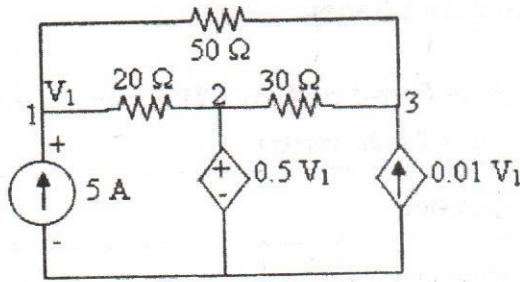
12. a) Use the nodal analysis to determine voltage at node 1 and the power supplied by the dependent current source in the network shown in figure:



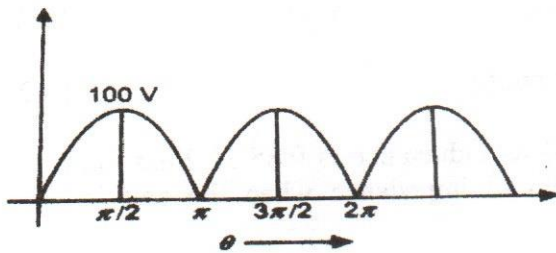- b) Find the rms value, average value and form factor of the voltage wave shown in figure:



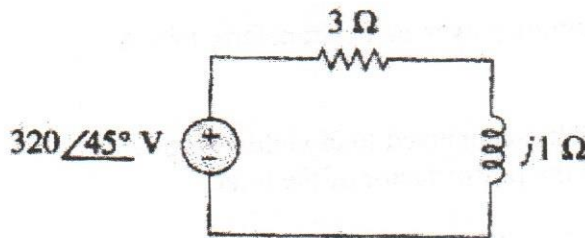
13. a) In the circuit shown in below figure, Calculate the average power absorbed by the resistor and inductor. Find the average power supplied by the voltage source.



- b) With a neat circuit diagram and phasor diagram, derive the expression for steady state current of a series RC circuit.
14. a) Explain the procedure to find thevenin's resistance of a circuit with DC excitation for both without dependent sources and with dependent sources.
- b) State and explain Norton's theorem.
15. a) Derive the expression for average three power in a three phase circuit.
- b) Three identical coils, each of resistance 10ohm and inductance 42mH are connected (a) in star and (b) in delta to a 415V,50 Hz, 3-phase supply. Determine the total power dissipated in each case

4	4	2	1,2,3
4	2	2	1,2
4	3	3	1,2,3
4	2	3	1,2
4	2	4	1,2
4	2	4	1,2
4	2	5	1,2
4	4	5	1,2,3

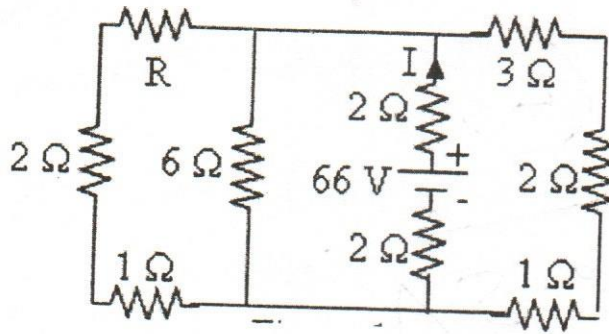16. a) Find the value of resistance R, if the current is  $I=11\text{ A}$  and source voltage is  $66\text{ V}$  as shown in figure:



4 3 1 1,2,3

- b) A series circuit consisting of a  $10\text{ ohm}$  resistor,  $100\text{ }\mu\text{F}$  capacitance and a  $10\text{ mH}$  inductance is driven by a  $50\text{ Hz}$  AC voltage source of maximum value  $100\text{ volts}$ . Calculate the equivalent impedance, current in the circuit, the power factor and power dissipated in the circuit.

4 3 2 1,2,3

17. Answer any *two* of the following:

- a) Two coils A and B are connected in series across a  $240\text{ V}$ ,  $50\text{ Hz}$  supply. The resistance of coil A is  $5\text{ ohms}$  and inductance of coil B is  $0.015\text{ H}$ . If input from the supply is  $3\text{ kW}$  and  $2\text{ kVAr}$ , find the resistance of coil B and inductance of coil A. Also calculate voltage across each coil.
- b) State and explain Superposition theorem with an example.
- c) With a neat circuit diagram and phasor diagram, explain the measurement of three phase power using two wattmeters in a three phase circuit.

4 3 3 1,2,3

4 2 4 1,2,3

4 2 5 1,2,3

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level - 1	20%
ii)	Blooms Taxonomy Level - 2	40%
iii)	Blooms Taxonomy Level - 3 & 4	40%

\*\*\*\*\*