

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 17342 S N/O

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (E.E.E.) VII-Semester Supplementary Examinations, May/June-2023

Electrical Drives and Static Control (PE-II)

Time: 3 hours

Max. Marks: 60

Note: Answer all questions from Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

Q. No.	Stem of the question	M	L	CO	PO
1.	What is the difference between a constant power drive and a constant torque drive?	2	1	1	1,2
2.	Define electric drive.	2	1	1	1,2
3.	Sketch the terminal voltage and armature current waveforms of a chopper operated separately excited dc motor.	2	1	2	1,2
4.	Draw a circuit to get the motoring operation of DC motor controlled by a chopper.	2	1	2	1,2
5.	Draw the circuit diagram of a single phase semi-converter control of a separately excited DC motor.	2	1	3	1,2
6.	Sketch the speed-torque characteristics of separately excited DC motor fed from a three phase fully controlled rectifier.	2	1	3	1,2
7.	Why V/f control should be preferred over only voltage control and only frequency control? Justify.	2	1	4	1,2
8.	Discuss, why the slip-power recovery scheme is suitable mainly for drives with a low speed range?	2	3	4	1,2,3
9.	What is slew range and ramping?	2	1	5	1,2
10.	Differentiate switched reluctance motor and synchronous reluctance motor.	2	3	5	1,2,3
Part-B (5 × 8 = 40 Marks)					
11. a)	Explain the closed loop speed control of electric drive with help of a block diagram.	4	2	1	1,2
b)	Discuss the factors for selection of an electric drive.	4	3	1	1,2
12. a)	Derive the expression for power regenerated by a separately excited dc motor connected to chopper during regenerative braking operation.	4	3	2	1,2
b)	With a neat circuit diagram, explain the operation of four quadrant chopper fed DC motor	4	2	2	1,2
13. a)	Derive the dynamic model of separately excited dc motor useful for speed control of dc motor drive.	4	3	3	1,2,3

Contd... 2

b)	<p>A 220 V, 1500 rpm, 11.6 A separately excited dc motor is controlled by a 1-phase fully controlled rectifier with an AC source voltage of 230 V, 50 Hz. Enough filter inductance is added to ensure continuous conduction for any torque greater than 25% of rated torque, $R_a = 2 \Omega$.</p> <p>i) What should be the value of the firing angle to get the rated torque at 1000 rpm?</p> <p>ii) Calculate the firing angle for the rated braking torque and -1500 rpm.</p> <p>iii) Calculate the motor speed at the rated torque and $\alpha = 160^\circ$ for the regenerative braking in the second quadrant.</p>	4	4	3	1,2,3
14. a)	<p>Explain the speed control of a three phase cyclo-converter fed induction motor drive.</p>	4	2	4	1,2
b)	<p>A three-phase 400V, 6-pole, 50Hz, delta-connected slip-ring induction motor has rotor resistance of 0.2Ω and leakage resistance of 1Ω/phase referred to stator. When driving a fan load it runs at full load at 4% slip. What resistance must be inserted in the rotor circuit to obtain a speed of 850 rpm. Neglect stator impedance and magnetizing branch. Stator to rotor turns ratio is 2.2.</p>	4	4	4	1,2,3
15. a)	<p>Describe the construction and operation of a brushless DC motor.</p>	4	2	5	1,2
b)	<p>Write the advantages and disadvantages of stepper motor.</p>	4	2	5	1,2
16. a)	<p>State essential parts of electrical drives. Discuss the functions of a power modulator.</p>	4	3	1	1,2
b)	<p>A 250V separately excited dc motor has an armature resistance of 2.5Ω. When driving a load at 600 rpm with constant torque, the armature takes 20 A. This motor is controlled by a chopper circuit with a frequency of 400 Hz and an input voltage of 250 V.</p> <p>i) What should be the value of the duty ratio if one desires to reduce the speed from 600 to 400 rpm, with the load torque maintained constant?</p> <p>ii) What should be the minimum value of the armature inductance, if the maximum armature current ripple expressed as a percentage of the rated current is not to exceed 10 percent?</p>	4	4	2	1,2,3
17.	<p>Answer any <i>two</i> of the following:</p>				
a)	<p>Explain in brief about the dual-converter control of dc motor. Also, derive the expression for firing angle if the dual-converter is operated in simultaneous control mode.</p>	4	2	3	1,2
b)	<p>Draw the circuit diagram of static Scherbius drive and explain the concept of slip recovery in brief.</p>	4	2	4	1,2
c)	<p>Discuss closed-loop speed control scheme for switched reluctance motor.</p>	4	3	5	1,2,3

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level - 1	20%
ii)	Blooms Taxonomy Level - 2	40%
iii)	Blooms Taxonomy Level - 3 & 4	40%
