

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 13458 S O

VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD

Accredited by NAAC with A++ Grade

B.E. (E.C.E.) III-Semester Supplementary Examinations, August-2023

Network Analysis and Transmission Lines

Time: 3 hours

Max. Marks: 60

Note: Answer all questions from **Part-A** and any **FIVE** from **Part-B**


Part-A (10 × 2 = 20 Marks)

Q. No.	Stem of the question	M	L	CO	PO/PSO
1.	State the maximum power transfer theorem	2	1	1	1, PSO 1
2.	Find the Y_{12} and Y_{21} parameters for the T network shown in below figure.	2	3	1	2, PSO 1
3.	What is the significance of initial conditions of energy storing elements in circuit analysis	2	1	2	1, PSO 1
4.	Differentiate between Zero State Response and Zero Input Response	2	2	2	1, PSO 1
5.	Determine the cut-off frequency of the constant k-filter given in the below figure.	2	3	4	2, PSO 1
6.	What is meant by resonance? Differentiate between series and parallel resonance circuits.	2	2	3	1, PSO 1
7.	Define wavelength and velocity of propagation of a transmission line	2	1	5	1, PSO 1
8.	How to eliminate the frequency distortion that occur in transmission lines	2	2	5	1, PSO 1
9.	Give the significance of Smith Chart.	2	1	6	1, PSO 1
10.	What is the value of characteristic impedance of a quarter wave transmission line to match 120 ohm load to the 75 ohm line	2	2	6	1, PSO 1


Contd... 2

Part-B (5×8 = 40 Marks)

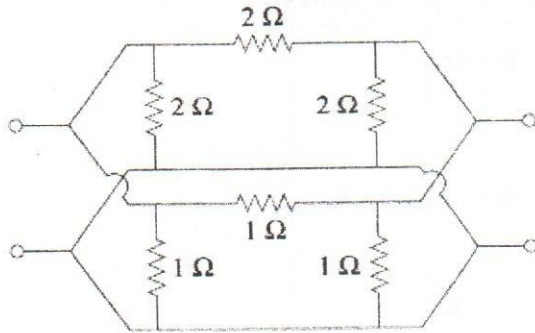11. a) Describe reciprocity theorem and derive the condition for reciprocity of a two port network 4 2 1 1, PSO 1
- b) Find the h parameters of the network given below. 4 3 1 2, PSO 1



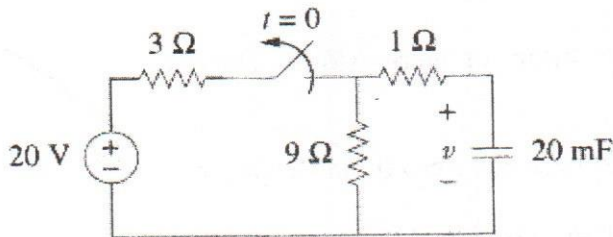12. a) Evaluate the time constant of an RL circuit. 4 2 2 1, PSO 1
- b) Find $v(t)$ for $t \geq 0$. Calculate the initial energy stored in the capacitor. 4 3 2 2, PSO 1




13. a) Design a T-section m-derived high pass filter with a cutoff frequency of $f_c = 20\text{KHz}$, design impedance of $400\ \Omega$ and given $m=0.2$. 4 3 4 2, PSO 1
- b) A series resonant circuit has $R=2\ \Omega$, $L=1\text{mH}$ and $C=0.3\ \mu\text{F}$. Determine the bandwidth, resonant frequency and Q factor when the input signal of $20\sin\omega t$ is applied. 4 3 3 2, PSO 1
14. a) Derive an input impedance expression for short and open circuited transmission lines 4 2 5 3, PSO 1
- b) The Characteristic Impedance of a uniform transmission line is $2039.6\ \Omega$ at a frequency of 800Hz . At this frequency the propagation constant was found to be $0.054\angle 87.9^\circ$. Determine the values of primary constants. 4 3 5 2, PSO 1
15. a) Determine the input impedance for $\lambda/2, \lambda/4, \lambda/8$ lines and brief their characteristics 4 2 6 3, PSO 1
- b) Compute the VSWR of a $75\ \text{ohm}$ transmission line when it is terminated by a load impedance of $50+j30\ \text{ohm}$ 4 3 6 2, PSO 1

16. a) Explain the impedance parameters and convert Z-parameters to h-parameters

4 1 1 1, PSO 1

b) The switch in the circuit of figure shown below has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ and V_L at $t = 1\text{ms}$.

4 3 2 2, PSO 1

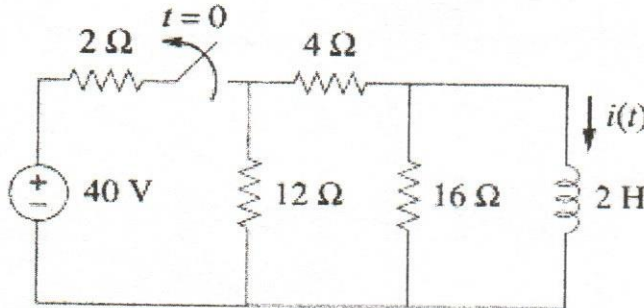

17. Answer any *two* of the following:

a) Draw the block diagram of composite filter and explain each block

4 1 4 1, PSO 1

b) Prove that a transmission line of finite length terminated by its characteristic impedance is equivalent to an infinite line.

4 2 5 3, PSO 1

c) Outline the significance of impedance matching and list various impedance matching devices used in transmission lines

4 2 6 1, PSO 1

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level - 1	20%
ii)	Blooms Taxonomy Level - 2	40%
iii)	Blooms Taxonomy Level - 3 & 4	40%
