



|        |   |   |   |   |         |
|--------|---|---|---|---|---------|
| 12. a) | Design a second order low pass Butterworth filter for cutoff of frequency of 1KHz .Assume C=1μF.      | 4 | 3 | 2 | 3, PSO1 |
| b)     | Explain the operation of Astable multivibrator using 555 timer.                                       | 4 | 1 | 3 | 2       |
| 13. a) | Design a voltage regulator using IC723 for an output of 5V and maximum load current of 25mA.          | 4 | 3 | 3 | 3, PSO1 |
| b)     | Describe the working of dual slope ADC with the help of neat circuit diagram.                         | 4 | 2 | 3 | 2       |
| 14. a) | Draw the diagram of 2-input standard TTL NAND gate and explain its working.                           | 4 | 2 | 4 | 2       |
| b)     | Compare TTL logic family with CMOS logic family.  | 4 | 3 | 4 | 2       |
| 15. a) | Design a 8-bit magnitude comparator using IC 7485.  | 4 | 3 | 5 | 3       |
| b)     | Design a Mod-8 counter using IC7490.  | 4 | 3 | 5 | 3, PSO1 |
| 16. a) | Design a lossy integrator using Op-Amp for an input signal frequency of 1KHz and pass band gain of 2. | 4 | 3 | 1 | 3       |
| b)     | Draw the block diagram of IC 8038 function generator and describe its working.                        | 4 | 2 | 3 | 2       |
| 17.    | Answer any <b>two</b> of the following:   |   |   |   |         |
| a)     | Explain the operation of inverted R-2R Ladder type DAC with an example.                               | 4 | 2 | 2 | 2       |
| b)     | Draw the circuit diagram of tri-state TTL NOT gate and explain its working.                           | 4 | 1 | 4 | 2, PSO1 |
| c)     | Design a pseudo random sequence generator using 4-bit shift register (IC7495).                        | 4 | 3 | 5 | 3       |

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

|      |                               |     |
|------|-------------------------------|-----|
| i)   | Blooms Taxonomy Level – 1     | 20% |
| ii)  | Blooms Taxonomy Level – 2     | 40% |
| iii) | Blooms Taxonomy Level – 3 & 4 | 40% |

\*\*\*\*\*