

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 11007 S

**VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD**  
**B.E. (CBCS) I-Semester Supplementary Examinations, June-2017**

**Basic Electrical Engineering**  
**(CSE, ECE & IT)**

Time: 3 hours

Max. Marks: 70


Note: Answer ALL questions in Part-A and any FIVE from Part-B

**Part-A (10 × 2 = 20 Marks)**

1. Define electric current, voltage, power and energy.
2. In a network consists of number of sources, to determine the current in a particular element which theorem is preferred, define that theorem.
3. Define active power and reactive power.
4. Define i) self inductance ii) mutual inductance.
5. What is the function of armature core in a d.c generator?
6. What is the significance of Back emf in a d.c motor?
7. Define regulation of a transformer.
8. What are the applications of auto transformer?
9. What factors do you consider while selecting a site for thermal power station?
10. Single phase motor is not self starting motor, explain.

**Part-B (5 × 10 = 50 Marks)**

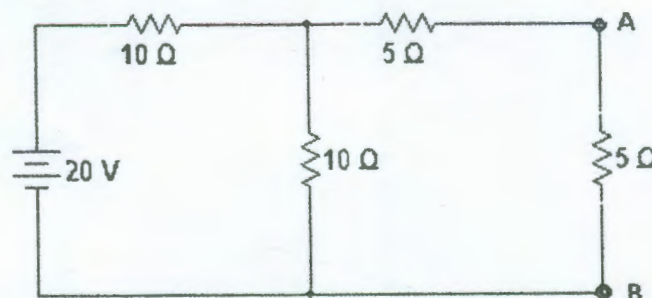11. a) Define Kirchoff's current law and voltage law. [4]  
b) Obtain the Thevenin's equivalent circuit and also find the current in 5 Ω resistor connected across AB. [6]



12. a) Derive the equation for energy stored in an inductance. [4]  
b) A 3-phase balanced star connected load consisting of  $5+j15\Omega$  in each phase is supplied from 415 V, 50 Hz 3-phase supply. Find i) phase current ii) line current iii) power factor iv) total power consumed. [6]
13. a) Derive the e.m.f equation of a d.c generator. [5]  
b) A 6 pole, 200 V lap wound d.c shunt motor armature has 600 conductors, a flux of 40 mWb and runs at a speed of 1200 r.p.m. It draws a line current of 40 A at full load. Its armature and field resistances are 0.2 Ω and 50 Ω respectively. Find its armature torque. [5]

14. a) Explain how equivalent circuit parameters are obtained by conducting suitable tests on a transformer. [5]  
b) Explain the construction and working principle of a 3-phase induction motor. [5]
15. a) Draw the layout of a hydro electric power plant. [5]  
b) Explain the construction of a single phase capacitor run motor. [5]
16. a) Define i) Thevenin's theorem ii) Norton's theorem. [5]  
b) Derive the relation between line and phase quantities in a 3-phase Delta connection. [5]
17. Write short notes on any *two* of the following:
- a) Characteristics of d.c compound motor. [5]  
b) Construction and principle of operation of auto transformer. [5]  
c) Nuclear power station. [5]

\*\*\*\*\*