

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No.: 22017ET AS

**VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD**  
B.E. (Civil Engg.) II Year II-Semester Advanced Supplementary Examinations, June/July-2017


**Electrical Technology**

Time: 1½ hours

Max. Marks: 35

**Part-A (11 Marks)**

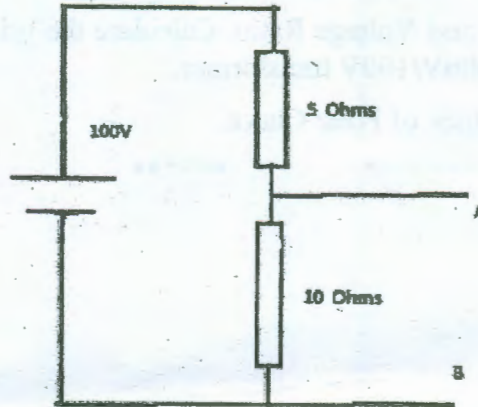
1. Write down the expression for power in a three phase balanced circuit. [1]
2. What are the different tests to conduct to find out the losses in a transformer? [1]
3. Can you name which type of induction motor is suitable in elevator and cranes? [1]
4. Draw the power triangle for a series RL circuit. [1]
5. Define  $\cos^3\theta$  law. [1]
6. What is the voltage across 10 ohm resistor in the figure below: [2]



7. Define regulation of a transformer and explain why does the regulation value should be low? [2]
8. A three phase, 50 Hz, induction motor has 6poles and operate with slip of 5% at certain load. Determine the synchronous speed and rotor frequency. [2]

**Part-B (3 × 8 = 24 Marks)**

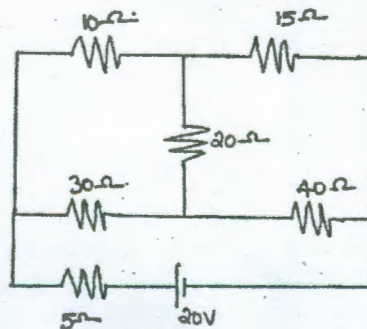9. a) A coil having a resistance of  $10\Omega$  and inductance of  $31.8\text{mH}$  is connected to  $230\text{V}$ ,  $50\text{Hz}$  supply. Calculate i) circuit current, ii) phase angle, iii) power factor, iv) voltage drop across the elements. [4]
- b) Calculate the power consumed in  $20\Omega$  resistor shown on the diag. [4]



10. a) Given below are the results conducted on 50KVA, 2200V/220V transformer. [4]  
 OC test (LV) : 405W, 5A, 220V  
 SC test (HV) : 805W, 20.2A, 95V  
 Calculate the parameters of the equivalent circuit referred to HV side.
- b) With help of phasor diagram explain the working of a Practical transformer under load condition. [4]
11. a) Explain about synchronous speed of a three phase induction motor which has 8 poles. [4]  
 If the full load slip is 2.5%, determine synchronous speed and rotor frequency of this motor working with 50Hz supply.
- b) Explain the concept of rotating magnetic field. [4]
12. Answer any two of the following:
- a) Derive the relationship between line voltage and phase voltage of a three phase star connected system. [4]
- b) Define Turns Ratio and Voltage Ratio. Calculate the primary side and secondary side current of 2KVA, 1000V/100V transformer. [4]
- c) Explain the significance of Polar Curve. [4]

\*\*\*\*\*

