

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 13206

VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD
B.E. (CSE: CBCS) III-Semester Main Examinations, December-2017

Logic & Switching Theory

Time: 3 hours

Max. Marks: 70

Note: Answer ALL questions in Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

1. Simplify the given function $f=(A+(BC)^1)^1 (AB^1+ABC)$
2. Determine the Sum of Minterms form for $F(x,y,z)=x^1y+z^1+xyz$
3. Implement EX-NOR gate using only NOR gates.
4. Implement the following Boolean function with NAND-NAND logic.
 $F(A,B,C)=\sum(0,1,3,5)$
5. Implement the following Boolean function using 4:1 multiplexer.
 $F(A,B,C)=\sum(1,3,5,6)$
6. Design a combinational logic circuit with three input variables that will produce a logic 1 output when more than one input variables are logic 1.
7. Compare Synchronous & Asynchronous Sequential Circuits.
8. Draw the logic diagram, logic symbol and Truth table of JK Flip flop.
9. Design a combinational circuit using ROM that accepts a 3-bit number and outputs a binary number equal to the square of the input number.
10. Draw the structure of PLA.

Part-B (5 × 10 = 50 Marks)

11. a) Prove using De-Morgans theorem that XOR and XNOR are complement to each other. [5]
b) Convert the following equation into the standard POS form. [5]
 $Y=(A+B)(A+C)(B+C^1)$.
12. a) Simplify the following function and find essential prime implicants. [6]
 $F(A,B,C,D)=\sum m(0,1,2,3,4,6,8,9,10,11)$
b) Implement $Y=AC+BC+AB+D$ with NOR-NOR logic. [4]
13. a) Design a 2 to 4 decoder using NOR gates only. [5]
b) Design a circuit with three inputs (A, B, C) and 2 outputs (X, Y), where the outputs are the binary count of the number of "ON" (HIGH) inputs. [5]
14. a) Design a sequence detector for the sequence 10110. Use JK Flip-Flop. [6]
b) Show how a JK flip flop can be constructed using a T flip flop and other logic gates. [4]
15. a) Derive the PLA program table for a combinational circuit that squares a 3-bit number. [5]
Minimize the number of product terms.
b) Construct a 128×8 ROM with four 32×8 ROM chips with an enable input, external connections and a decoder. [5]

16. a) Find the complement of $f=A+(B+C^1).D+E^1$ F. [4]
b) Express the following functions in sum of min terms and product of max terms. [6]
i) $F(A,B,C) = 1$ ii) $F(A,B,C) = (AB+C)(B+AC)$

17. Answer any **two** of the following:

- a) Explain the design procedure for combinational circuits. [5]
b) Design a 3-bit UP/DOWN counter which counts up when the control signal $M=1$ and counts down when $M=0$. [5]
c) Write short notes on Programmable Array Logic. [5]

