

- 16. a) Simplify the function $F(A,B,C,D) = (0,2,6,11,12,13,14)$ using k-maps and implement the circuit using NAND gate only. [6]
- b) Implement EX-OR gate using NAND gates and NOR gates. [4]
- 17. Answer any *two* of the following:
 - a) Design a circuit with four inputs and one output where the output is 1 if the input is divisible by 3 or 7. [5]
 - b) Design a Modulo-7 binary counter using J K Flip-Flop. Draw its state diagram. [5]
 - c) Explain AND-OR structure of PLA & PAL. [5]

