

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 22201

**VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD**  
**B.E. II Year (E.E.E.) II-Semester (Main) Examinations, May-2016**

**Electrical Circuits-II**

Time: 3 hours

Max. Marks: 70

Note: Answer ALL questions in Part-A and any FIVE from Part-B

**Part-A (10 × 2 = 20 Marks)**

- The current in an RLC circuit is described by:  $\frac{d^2i}{dt^2} + 10 \frac{di}{dt} + 25i = 0$   
 If  $i(0) = 10$  and  $\frac{di(0)}{dt} = 0$ , find  $i(t)$  for  $t > 0$ .
- If  $R = 20 \Omega$ ,  $L = 0.6$  H, what value of  $C$  will make an RLC series circuit :  
 i) Over damped      ii) Critically damped
- Determine the Laplace transform of each of the following functions:  
 i)  $u(t)$       ii)  $e^{-at} u(t)$ ,  $a \geq 0$
- State and prove initial value theorem.
- When the input to a system is a unit step function, the response is  $10 \cos 2t$ . Obtain the transfer function of the system.
- Draw the series equivalent circuit of inductor in s-domain.
- State the differentiation theorem of fourier transform.
- Find the fourier transform of  $\sin \omega_0 t$  and  $\cos \omega_0 t$ .
- Draw the first cauer form of RL representation.
- List the properties of LC reactance functions.

**Part-B (5 × 10 = 50 Marks)**

11. Find  $i(t)$  for  $t > 0$  for the circuit shown in fig.1. [10]


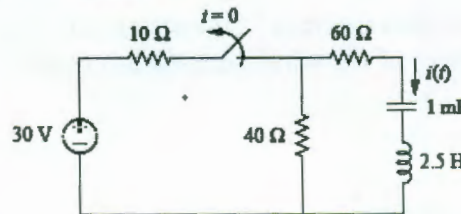


Fig. 1

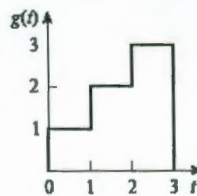12. a) State and prove the properties of Laplace transform given below: [5]  
 i) Linearity      ii) Time shift      iii) Time differentiation
- b) Obtain the Laplace transforms of the functions shown in Fig.2 [5]



(a)  
Fig. 2

13. a) For the circuit in Fig. 3(a), Find  $i(t)$  for  $t > 0$  if  $i(0) = 2A$ . [5]  
 b) Obtain the transfer function  $H(s) = V_o(s)/I(s)$  for the circuit of Fig. 3(b) [5]

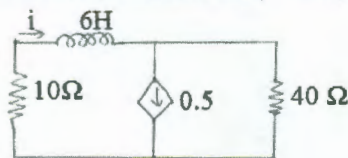


Fig. -3 (a)

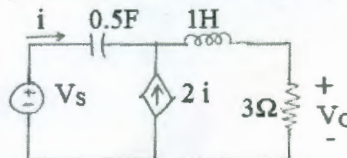


Fig. -3 (b)

14. a) Find the Fourier transform of the function shown in fig.4. [5]

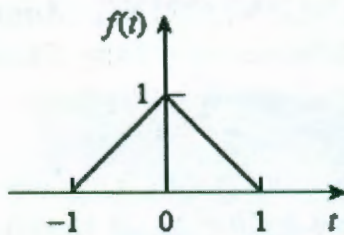


Fig. 4

b) Determine the fourier transform of  
 i) the double-sided exponential  $e^{-a|t|}$  and ii) the signum function  $\text{sgn}(t)$ . [5]

15. a) Explain the significance of elements in the foster form. [5]

b) Identify whether the following polynomial is Hurwitz. [5]

$$P(s) = s^6 + 4s^5 + 8s^4 + 20s^3 + 19s^2 + 16s + 12$$

16. a) For the circuit in Fig.5, calculate the value of R needed to have a critically damped response. [5]

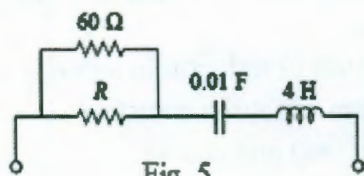


Fig. 5

b) Determine the inverse Laplace Transforms of (i)  $\frac{4}{(s+1)(s+3)}$  (ii)  $\frac{12}{(s+2)^2(s+4)}$  [5]

17. Answer any **two** of the following:

a) Using Laplace Transforms determine  $i_x$  in the circuit of Fig. 6 [5]

b) Determine the Fourier series of the waveform shown in fig. 7 [5]

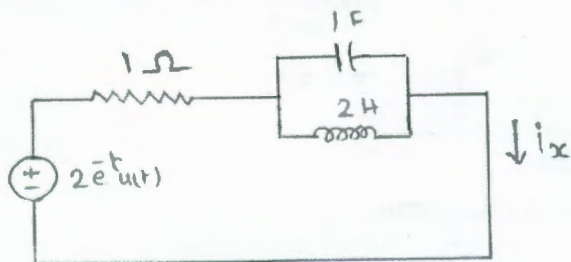


Fig (6)

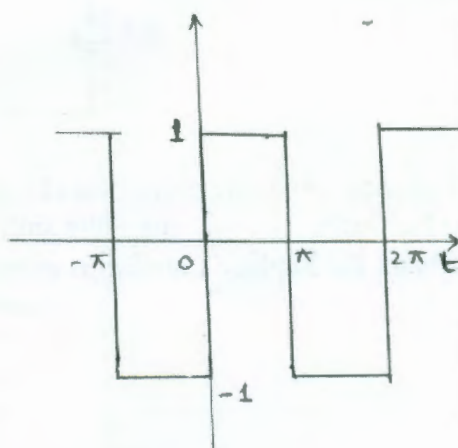


Fig (7)

c) Synthesize:  $Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$  using cauer forms. [5]

\*\*\*\*\*