

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 22201

VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD
B.E. II Year (E.E.E.) II-Semester (Main) Examinations, May-2016

Electrical Circuits-II

Time: 3 hours

Max. Marks: 70

Note: Answer ALL questions in Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

- The current in an RLC circuit is described by: $\frac{d^2i}{dt^2} + 10\frac{di}{dt} + 25i = 0$
 If $i(0) = 10$ and $\frac{di(0)}{dt} = 0$, find $i(t)$ for $t > 0$.
- If $R = 20 \Omega$, $L = 0.6 \text{ H}$, what value of C will make an RLC series circuit :
 i) Over damped ii) Critically damped
- Determine the Laplace transform of each of the following functions:
 i) $u(t)$ ii) $e^{-at} u(t)$, $a \geq 0$
- State and prove initial value theorem.
- When the input to a system is a unit step function, the response is $10 \cos 2t$. Obtain the transfer function of the system.
- Draw the series equivalent circuit of inductor in s-domain.
- State the differentiation theorem of fourier transform.
- Find the fourier transform of $\sin \omega_0 t$ and $\cos \omega_0 t$.
- Draw the first cauer form of RL representation.
- List the properties of LC reactance functions.

Part-B (5 × 10 = 50 Marks)

11. Find $i(t)$ for $t > 0$ for the circuit shown in fig.1. [10]


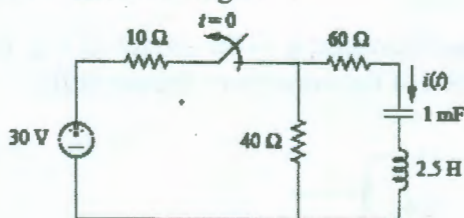


Fig. 1

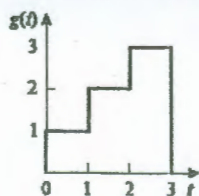12. a) State and prove the properties of Laplace transform given below: [5]
 i) Linearity ii) Time shift iii) Time differentiation
- b) Obtain the Laplace transforms of the functions shown in Fig.2 [5]



(a)
Fig. 2

13. a) For the circuit in Fig. 3(a), Find $i(t)$ for $t > 0$ if $i(0) = 2A$. [5]
 b) Obtain the transfer function $H(s) = V_0(s)/I(s)$ for the circuit of Fig. 3(b) [5]

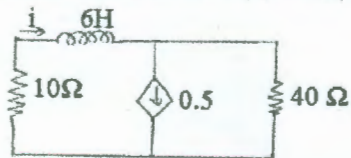


Fig. -3 (a)

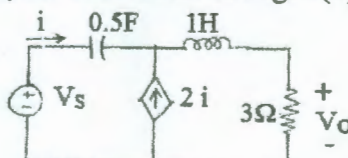


Fig. -3 (b)

14. a) Find the Fourier transform of the function shown in fig.4. [5]

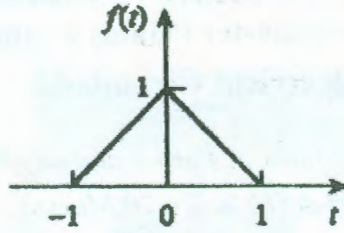


Fig. 4

- b) Determine the fourier transform of [5]
 i) the double-sided exponential $e^{-a|t|}$ and ii) the signum function $\text{sgn}(t)$.
 15. a) Explain the significance of elements in the foster form. [5]
 b) Identify whether the following polynomial is Hurwitz. [5]
 $P(s) = s^6 + 4s^5 + 8s^4 + 20s^3 + 19s^2 + 16s + 12$
 16. a) For the circuit in Fig.5, calculate the value of R needed to have a critically damped response. [5]

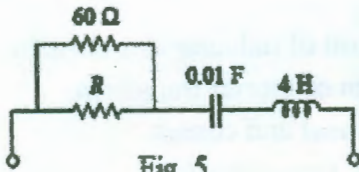


Fig. 5

- b) Determine the inverse Laplace Transforms of (i) $\frac{4}{(s+1)(s+3)}$ (ii) $\frac{12}{(s+2)^2(s+4)}$ [5]
 17. Answer any two of the following:
 a) Using Laplace Transforms determine i_x in the circuit of Fig. 6 [5]
 b) Determine the Fourier series of the waveform shown in fig. 7 [5]

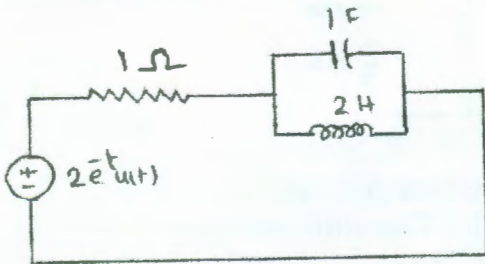


Fig (6)

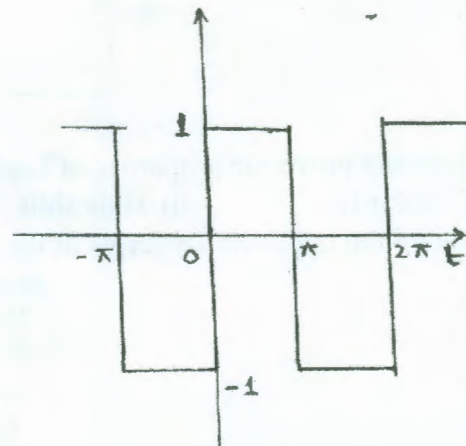


Fig (7)

- c) Synthesize: $Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$ using cauer forms. [5]
