

12. a)	Give the detail classification of DC machine and draw the cross sectional view of the DC machine.	3	2	2	1,2
b)	A six pole DC generator has 150 slots and each slot has 8 conductor with resistance of each conductor is $.015\Omega$. The armature current is 20A. Calculate current per conductor and drop in armature for wave and lap winding connection?	5	4	2	1,2
13. a)	With a neat sketch explain about 4-point starter for starting of DC shunt motor.	4	2	3	1,2
b)	A 250V DC shunt motor running at 750 rpm takes armature current of 45A. The armature resistance is 0.3Ω . What resistance must be placed in series with armature to reduce the speed to 600 rpm, assume the torque remain constant.	4	4	3	1,2
14. a)	Explain the working principle of transformer and derive the expression for EMF generated in a transformer winding.	3	2	4	1,2
b)	The OC and SC test data of 5 KVA, 250/500V single phase transformer when supplying full load at 0.8 lagging p.f is given below. OC test: 250V, 0.8A, 70W(HV open circuit) SC test: 20V, 10A, 60W (L V short circuit) calculate efficiency at (a) full load (b) half load (c) voltage regulation at full load	5	4	4	1,2
15. a)	Explain how the Auto-transformer makes effective saving on copper and copper losses, when its transformation ratio is less than 2?	4	2	5	1,2
b)	A 25kVA, 2000/200 V, 2-winding transformer is to be used as an autotransformer with constant source voltage of 2000 V. at full load of unity power factor, calculate the auto transformer output power, power transferred by conduction and induction. If the efficiency of the 2-winding transformer at 0.8 power factor is 95%, find the efficiency of the auto transformer at same load and same power factor.	4	4	5	1,2
16. a)	Derive an expression for self-Inductance and mutual Inductance?	4	2	1	1,2
b)	A four pole Lap wound shunt generator supplies 60 lamps of 100W, 240V each, the field and armature resistance 55 ohm and 0.18 ohm respectively. If the brush drop is 1V in each brush. Find armature current and generated EMF?	4	4	2	1,2
17.	Answer any <i>two</i> of the following:				
a)	A DC series motor is running with the speed of 1000 RPM draws a current of 40 A from a 250 V supply. If the load is changed such that the current drawn by the motor is increased to 70 A, calculate the speed of a motor on new load. The armature and series field winding resistance are 0.25ohms and 0.35ohms respectively. Assume the flux produced is proportional to the current.	4	4	3	1,2
b)	Explain parallel operation of single phase transformer and write the necessary conditions for the parallel operation of the transformers.	4	2	4	1,2
c)	Draw and explain the significance of Y-Y, Y-delta, Delta-Y, and Delta-Delta connection in 3-phase transformers?	4	2	5	1,2

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level – 1	20
ii)	Blooms Taxonomy Level – 2	40
iii)	Blooms Taxonomy Level – 3 & 4	40