

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 14345

**VASAVI COLLEGE OF ENGINEERING (AUTONOMOUS), HYDERABAD***Accredited by NAAC with A++ Grade***B.E. (E.E.E.) IV-Semester Main & Backlog Examinations, July-2022****Electronics Engineering-II**

Time: 3 hours

Max. Marks: 60

*Note: Answer all questions from Part-A and any FIVE from Part-B***Part-A (10 × 2 = 20 Marks)**

Q. No.	Stem of the question	M	L	CO	PO
1.	Define linear wave shaping?	2	1	4	1
2.	What is the difference between clipping and clamping?	2	1	5	1
3.	List out the advantages and disadvantages of multistage amplifiers?	2	2	1	1
4.	Define CMRR of a differential amplifier?	2	1	3	1
5.	List out the advantages of negative feedback in an amplifier?	2	2	1	1
6.	What is the effect of negative feedback on a bandwidth?	2	3	1	1
7.	State the conditions for sustained oscillations.	2	1	2	1
8.	A crystal oscillator has the highest frequency stability. Justify.	2	3	2	1
9.	Classify the amplifiers based on the operating point selection?	2	2	1	1
10.	How the efficiency of class A power amplifier is improved by the transformer coupled amplifier configuration?	2	3	1	1
<b>Part-B (5×8 = 40 Marks)</b>					
11. a)	Derive the expression for output voltage when ramp signal applied to an RC high pass circuit?	4	3	4	1
b)	Design a diode clamper to restore the positive peaks of 1 KHz input signal to a voltage level equal to 5 V.	4	4	5	3
12. a)	Explain the operation of a direct couple amplifier.	4	2	1	1
b)	Three identical cascaded amplifier stages have overall upper 3 dB frequency of 100 KHz and overall lower 3 dB frequency of 20 Hz. Find the upper and lower 3 dB frequency of individual stages.	4	3	1	2
13. a)	Draw the block diagram of a voltage series feedback amplifier and derive the expressions for voltage gain and output impedance with feedback?	5	1	1	1
b)	An amplifier with open loop voltage gain of $1000 \pm 50\%$ is available. Determine the closed loop voltage gain and the feedback factor if the gain is altered by $\pm 0.1\%$ .	3	3	1	2

14. a)	Derive the expression for frequency of oscillation of a Colpitts oscillator?	5	4	2	1
b)	An RC phase shift oscillator employing BJT with $R = 200 \text{ K}\Omega$ and $C = 200 \text{ pF}$ . Determine the frequency of the oscillator.	3	3	2	2
15. a)	Explain the operation of class A power amplifier with neat sketches?	4	1	1	1
b)	A sinusoidal signal $V_s = 1.95 \sin 400t$ is applied to a power amplifier. The resulting current is $i = 12 \sin 400t + 1.2 \cos 800t + 0.9 \sin 1200t$ . Determine the total harmonic distortion.	4	3	1	2
16. a)	With neat diagram, explain the operation of single level clipping circuit with positive reference voltage.	4	2	5	1
b)	Discuss the frequency response of RC coupled amplifier with neat sketches?	4	3	1	1
17.	Answer any <i>two</i> of the following:				
a)	What is negative feedback? Discuss how it effects on input and output impedance of an amplifier.	4	2	1	1
b)	Explain the frequency stability criteria for sinusoidal oscillators?	4	2	2	1
c)	Explain the operation of Class – B Complementary symmetry Power amplifier.	4	2	1	1

M : Marks; L: Bloom's Taxonomy Level; CO; Course Outcome; PO: Programme Outcome

i)	Blooms Taxonomy Level – 1	23.6%
ii)	Blooms Taxonomy Level – 2	36.1%
iii)	Blooms Taxonomy Level – 3 & 4	40.3%

\*\*\*\*\*