

**VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD**  
**B.E. II Year (E.C.E.) I-Semester Supplementary Examinations, May/June-2017**

**Basic Circuit Analysis**


Time: 3 hours

Max. Marks: 70

*Note: Answer ALL questions in Part-A and any FIVE from Part-B*

**Part-A (10 X 2=20 Marks)**

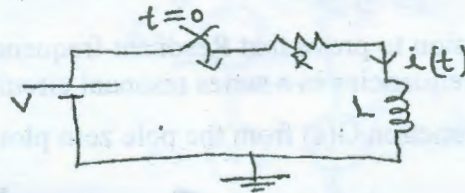
1. State and Explain the Volt-Ampere relationships for R, L and C components.
2. Distinguish between Independent and dependent sources.
3. State and explain Norton's theorem.
4. Find the expression for current  $i(t)$  in the circuit shown below for  $t > 0$ .




5. "The Current through an inductor cannot change instantaneously". Explain and justify the statement.
6. A coil with 1500 turns surrounds a magnetic circuit which has a reluctance of  $6 \times 10^{-6}$  AT/wb. Calculate the inductance of the coil.
7. Define power Factor.
8. Define Q-factor of a resonant circuit.
9. What is Duality? Sketch dual of simple RLC network.
10. State properties of Tieset analysis.

**Part-B (5 × 10 = 50 Marks)**

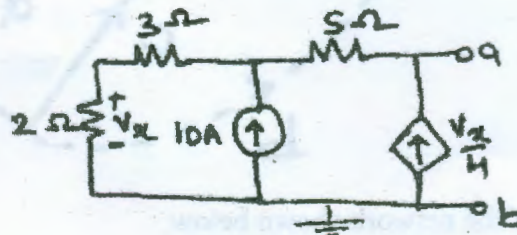11. a) Obtain Thevenin's equivalent network across the terminals a and b for the network shown below. [6]




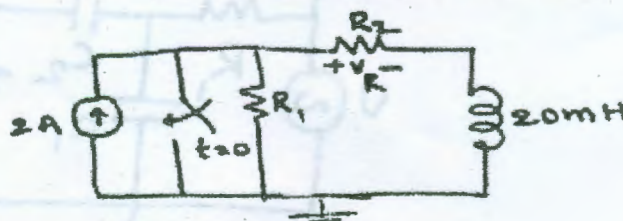- b) State and prove Reciprocity theorem using a simple network. [4]
12. a) Select values of  $R_1$  and  $R_2$  in the circuit so that  $V_R(0+) = 10$  V and  $V_R(\text{lms}) = 5$  V. [7]




- b) Illustrate the Steady state behaviour of Inductor and Capacitor. [3]

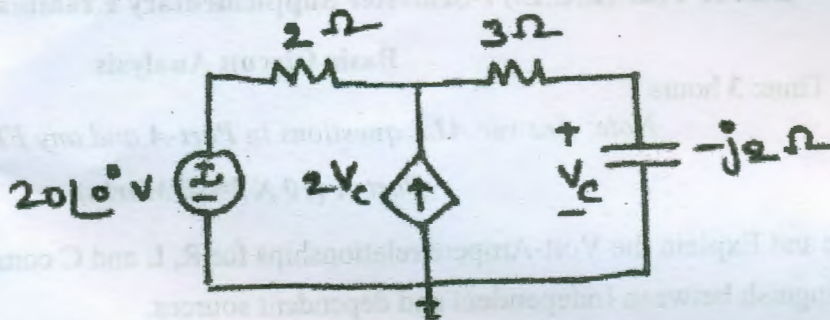
13. a) Determine Average power supplied by dependent source in the circuit. [5]



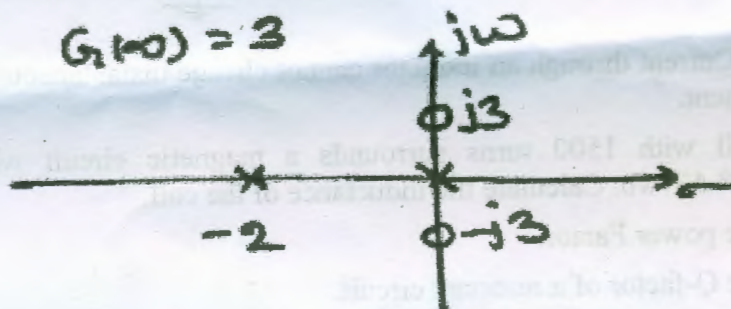
- b) Find complex voltage across series combination of a 500 Ω resistor and a 900 mH inductor if complex current  $8e^{j3000t}$  mA flows through two elements in series. [5]
14. a) Derive an expression to prove that Resonant frequency is equal to geometric mean of two half power frequencies in a series resonant circuit. [6]
- b) Obtain transfer Function  $G(s)$  from the pole zero plot. [4]



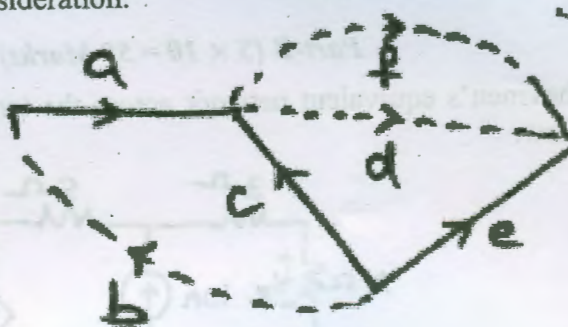15. a) Obtain Fundamental Tie-Set matrix of the network graph shown below taking tree branches a,c,e into consideration. [5]




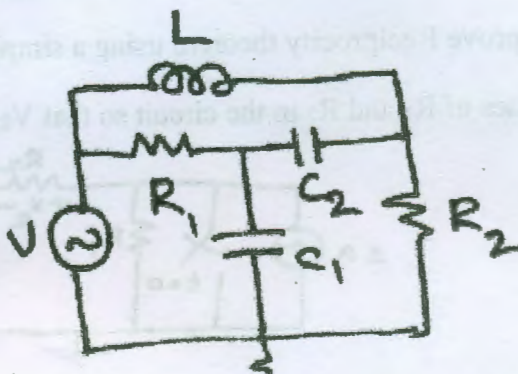- b) Obtain dual of the network shown below. [5]




16. a) If  $I_L(0) = 10 \text{ A}$  in the circuit shown, Find  $I_L(t)$  for  $t > 0$ .

[5]

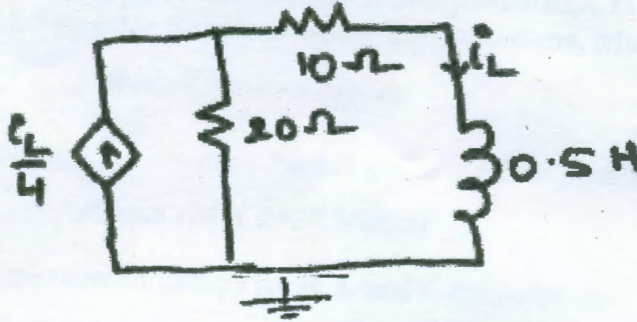

b) Determine voltage across terminals AB in the circuit shown below:

[5]

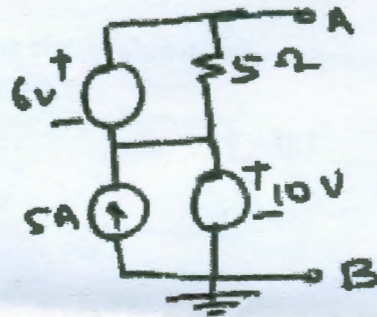

17. Write short notes on any two of the following:

a) Reactive power

[5]

b) Co-efficient of Coupling

[5]

c) ZIR and ZSR.

[5]

\*\*\*\*\*