

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD**  
**B.E. (ECE: CBCS) III-Semester Supplementary Examinations, June-2019**

**Networks Analysis**


Time: 3 hours

Max. Marks: 60

*Note: Answer ALL questions in Part-A and any FIVE from Part-B*

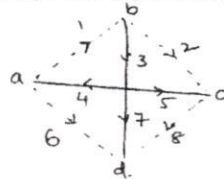**Part-A (10 × 2=20 Marks)**

- State and explain Kirchoff's Laws
- Obtain fundamental cut-set matrix for the network graph shown in figure




- State Tellegen's theorem.
- Obtain the Thevenin's equivalent circuit for the network shown in figure




- Differentiate between Zero Input Response (ZIR) and Zero State Response.
- How to evaluate the initial conditions of a circuit?
- Define Z-parameters of the network
- Draw the equivalent circuit for the h-parameters.
- Check whether the given polynomial  $P(S)=S^4 + S^3 + 2S^2 + 4S + 1$  is Hurwitz or not
- Define Bandwidth of a resonant circuit and draw the frequency response of an RLC series circuit.

**Part-B (5 × 8=40 Marks)**

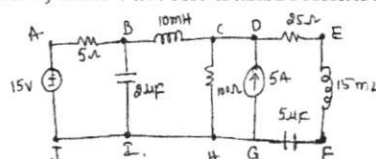- a) For the electrical network shown in figure, draw its topological graph and write its incidence matrix, tie-set matrix, link current transformation equation and branch current [4]




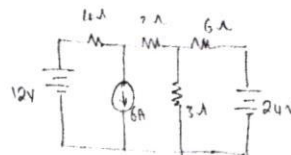- b) Use Source transformation to find  $I_o$  in the circuit shown in figure [4]




- a) Explain the step by step procedure for obtaining the Thevenin's equivalent of a given circuit with an example. [3]

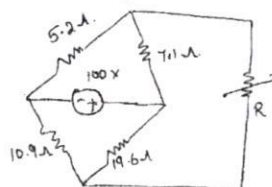
- b) Find the value of R that receive maximum power. Determine the maximum power. [5]



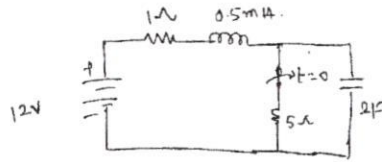
13. a) The switch shown in the following circuit has been closed for a very long time. It opens at  $t=0$ . Find  $V_C(t)$  for  $t>0$  using differential equation approach [5]



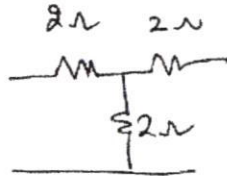- b) Differentiate between transient and steady state analysis. [3]
14. a) Find the transmission parameters for the network shown below [4]




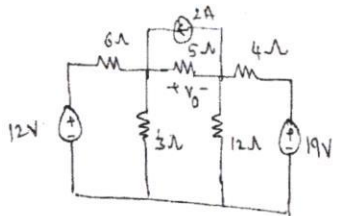- b) Derive the relation between Z-parameters and h-parameters. [4]
15. a) Realize the function  $Z(S) = \frac{S(S^2+4)}{2(S^2+1)(S^2+9)}$  in Foster form-I LC network. [4]
- b) Realize the function  $Z_{RC}(S) = \frac{S^2+4S+1}{(4S^2+5S+1)}$  in Cauer -II form. [4]
16. a) Distinguish between mesh and Nodal analysis. [3]
- b) By Super-position theorem calculate current I in the following circuit. [5]



17. Answer any **two** of the following:

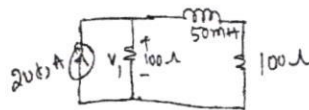- a) For the circuit shown in figure, find the values of  $V_1$  at  $t$  equal to (a)  $0^-$  (b)  $0^+$  (c)  $\infty$  (d) 0.2msec [4]



- b) Show that when two 2-port networks N1 and N2 are connected in parallel, the equivalent Y-parameters of the combined network is the sum of Y-parameters of each individual 2-port network. [4]
- c) For the circuit shown in figure, determine the Q factor value at resonance and bandwidth of the circuit [4]

