

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No.: 22303 S

VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD
B.E. II Year (E.C.E.) II-Semester (Supplementary) Examinations, December-2016

Networks and Transmission Lines

Time: 3 hours

Max. Marks: 70

Note: Answer ALL questions in Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

1. Distinguish between Symmetrical and Asymmetrical networks.
2. Define image impedance and iterative impedance.
3. Design a constant k-type LPF for cut off frequency of 1 KHz with nominal impedance 600Ω.
4. Draw a general block diagram for Composite filter.
5. Design a symmetrical T- attenuator for $R_o = 600$ Ohms and attenuation of 20 dB.
6. Test whether the given polynomial $S^4 + 5S^3 + 8S^2 + 9S + 6$, is Hurwitz or not.
7. Define the primary constants of a transmission line.
8. Determine the VSWR of a transmission line when load is short circuit and under matched condition.
9. What are the differences between single and double stub matching?
10. How is VSWR related to Reflection Co-efficient?

Part-B (5 × 10 = 50 Marks)

11. a) Derive expressions for image and iterative impedances of a symmetrical T-network. [5]
b) An impedance matching network is to operate between resistances 100 Ω and 500 Ω. [5]
having a image phase constant of 63.4° . Compute the insertion loss and insertion ratio of the network.
12. a) Find the circuit elements of a prototype high pass T-section filter having cut-off frequency [6]
of 1,000 Hz to work into a 600 Ohms load resistance.
b) What are the limitations of constant K filters? How to overcome by using m - derived [4]
sections?
13. a) Design an asymmetrical L-attenuator to work into design impedance of 400 Ω and 300 Ω. [5]
b) Derive an expression for input impedance of a line of finite length. [5]
14. a) Derive the condition for a distortion less transmission line and explain how loading of [6]
cables helps to achieve this condition.
b) Impedance measurements made on a $\frac{1}{4}$ Km length of a cable at 1.6 KHz under open and [4]
short circuit conditions have $Z_{oc} = 2460 \angle -86.5^\circ$, $Z_{sc} = 21.5 \angle 11^\circ$. Calculate Z_o , α
(alternation constant) and β (Phase constant).
15. a) A lossless transmission line whose characteristic impedance is 50 Ω and which is [6]
terminated by the load $100 + j150$ Ω. Determine length of the short circuit stub to match the
load using Smith chart.
b) Write applications of Smith Chart. [4]
16. a) Derive the expression for the characteristic impedance and propagation constant for [6]
asymmetrical π -network.
b) List out the merits and demerits of m-derived filters. [4]
17. Write short notes on any **two** of the following:
a) Equalizers [5]
b) Phase velocity and Group Velocity. [5]
c) Properties of transmission lines at UHF. [5]
