

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 22314

**VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD**  
**B.E. (E.C.E.) II Year II-Semester Main & Backlog Examinations, May-2017**

**Networks and Transmission Lines**


Time: 3 hours

Max. Marks: 70

Note: Answer ALL questions in Part-A and any FIVE from Part-B

**Part-A (10 × 2 = 20 Marks)**

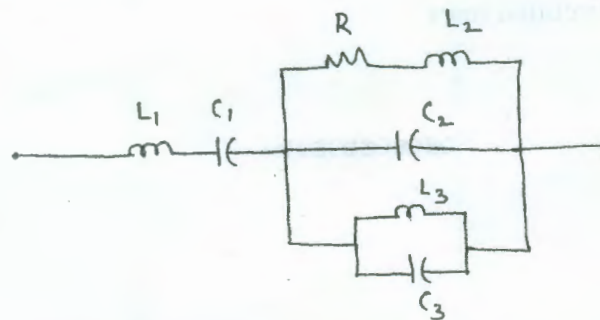1. List out the functional classifications of networks.
2. The impedance of a series and shunt arms of L network are  $j300$  ohms and  $-j700$  ohms respectively. Calculate iterative impedances of the network.
3. What are the advantages of 'm' derived filters?
4. Determine the circuit elements of a prototype high pass T section filter having cut off frequency of 1000 Hz to work into a 600 ohm load resistance.
5. List out the classifications of attenuators.
6. For a given network, draw its inverse network.



7. Define primary constants and secondary constants of a transmission line.
8. Write the properties of transmission lines.
9. What are the drawbacks of Quarter wave transmission line impedance matching technique?
10. Distinguish between open and short circuit stubs.

**Part-B (5 × 10 = 50 Marks)**

11. a) Explain the electrical characteristics of a symmetrical network. [5]  
b) Derive characteristic impedance and propagation constant expressions for symmetrical  $\pi$  network. [5]
12. a) Explain constant-K bandpass filter and derive its design equations. [5]  
b) Design an m derived T section low pass filter having cut off frequency  $f_c = 1000$  Hz, design impedance  $R_k = 600$  ohms and frequency of infinite attenuation  $f_\infty = 1050$  Hz. [5]
13. a) Synthesize the given driving point impedance function  $Z_{RL}(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$  in Foster form I and II realizations. [5]  
b) Write the properties of Positive real function and Test whether the given function  $F(s) = \frac{s+5}{s^3+3s^2+2s+1}$  is PRF or not. [5]

14. a) Prove that for a transmission line  $Z_o = \sqrt{Z_{sc} Z_{oc}}$ . [6]  
 b) Explain about loading of cables. [4]
15. A lossless transmission line whose characteristic impedance is  $150 \Omega$  and which is terminated by  $150 + j300 \Omega$  load. Using Smith Chart determine [10]  
 a) Reflection Coefficient at distance of  $0.3 \lambda$  from the load  
 b) VSWR,  $R_{max}$  and  $R_{min}$  on the transmission line  
 c) Impedance at a distance of  $0.8 \lambda$  from the load  
 d) Convert load impedance into admittance.
16. a) Design symmetrical lattice network for the following specifications Characteristic impedance  $Z_o = 600 \Omega$  and propagation constant  $\gamma = j \frac{\pi}{8}$  [5]  
 b) Explain about composite filter with a neat block diagram. [5]
17. Write short notes on any *two* of the following:  
 a) Hurwitz polynomials [5]  
 b) Open and short circuited lines [5]  
 c) Stub matching. [5]

XXXXXXXXXX