

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No.: 22315 AS

VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD
B.E. (E.C.E.) II Year II-Semester Advanced Supplementary Examinations, June/July-2017

Pulse, Digital and Switching Circuits

Time: 3 hours

Max. Marks: 70

Note: Answer ALL questions in Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

1. Show that a Lowpass RC circuit acts as an integrator.
2. Mention the effects of diode characteristics on clamping voltage.
3. Compare conventional Bi-stable Multi-vibrator and Schmitt trigger circuits.
4. Sketch all the wave forms of collector coupled Mono-stable Multi-vibrator when it is in stable and quasi stable state.
5. Realize EX-OR and EX-NOR gates using minimum number of NAND gates.
6. Implement a half adder with two 2x1 multiplexers and NOT gates.
7. Write the function for the carry outputs of each stage of a four bit Carry Look Ahead adder.
8. Construct JK Flip flop using D flip flop, a 2 to 1 multiplexer and an inverter.
9. Differentiate among Synchronous and Asynchronous sequential circuits.
10. A machine has to detect a sequence 1010, obtain its state diagram. (over lapping allowed).

Part-B (5 × 10 = 50 Marks)

11. a) Explain the operation of an RLC circuit when a step input is applied at its inputs (with initial condition equal to be zero) as a function of K. [5]
b) The limited ramp is applied to an RC differentiator as shown in fig. 11 b. Draw to scale the output wave form for the cases $T = RC$, $T = 0.2 RC$ & $5 RC$. [5]

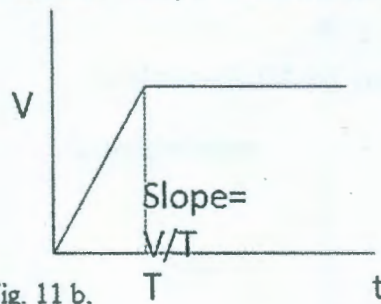


Fig. 11 b.

12. a) Derive an expression for gate / pulse width of an emitter coupled Mono-stable Multi-vibrator. [4]
b) Describe the operation of a Schmitt trigger circuit and derive expressions for UTP and LTP. [6]
13. a) Express the compliment of the following function in product of sum form $F(A,B,C,D) = \sum(3,5,9,11,15)$. [3]
b) Draw a logic diagram using only two input NOR gates to implement the following function $f(A,B,C,D) = (A \text{ XNOR } B) (C \text{ XOR } D)$. [4]
c) Implement the Boolean function $F(A,B,C,D) = \sum(1,3,4,11,12,13,14,15)$ using Multiplexer. [3]

14. a) Reduce the given state diagram and perform state assignment. [6]

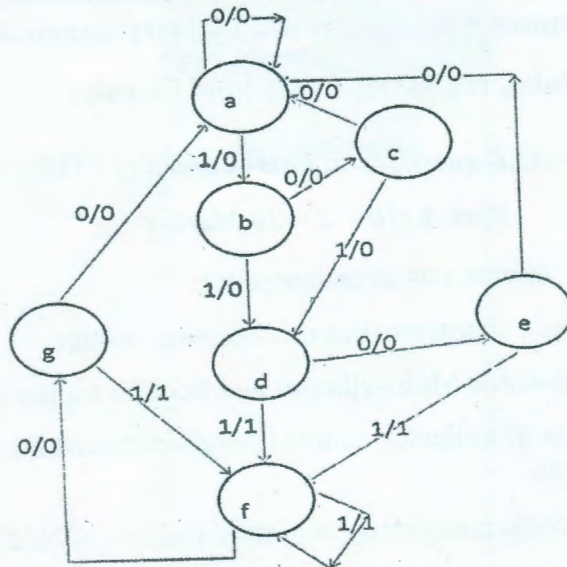


Fig. 14 a.

b) Draw the truth table of priority encoder and differentiate it with normal encoder. [4]

15. a) Design 4-bit UP/DOWN counter. Use one control signal to select either to perform UP counting or DOWN counting. Mealy type of modelling and JK flip-flops has to be used. [6]

b) Draw the block diagram of universal shift register. [4]

16. a) Explain about linear and non-linear wave shaping circuits. [5]

b) Design a sweep circuit using UJT to trigger TRIAC. [5]

17. Write short notes on any *two* of the following: [5]

a) Static Hazards [5]

b) Ring counter [5]

c) Designing procedure for Mealy machine. [5]

