

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 13414

**VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD**  
**B.E. (ECE: CBCS) III-Semester Main Examinations, December-2018**

**Networks Analysis**


Time: 3 hours

Max. Marks: 60

Note: Answer ALL questions in Part-A and any FIVE from Part-B

Q. No	Stem of the Question	M	L	CO	PO
<b>Part-A (10 × 2 = 20 Marks)</b>					
1.	Define Twig, Co-tree.	2	2	1	2
2.	Transform the following circuit into a single current source.	2	2	1	3
3.	State Thevenin's and Norton's theorems and also write their limitations	2	2	2	2
4.	State Maximum Power transfer theorem.	2	2	2	2
5.	Write the procedure to evaluate the initial conditions of during the transient analysis of circuits.	2	2	3	2
6.	Differentiate between Zero Input Response (ZIR) and Complete Response.	2	2	3	2
7.	Draw the equivalent circuit of a two-port network in terms Y-parameters and g-parameters.	2	2	4	2
8.	Find Admittance parameters of the circuits given below:	2	2	4	3
9.	List the properties of Positive Real Functions.	2	2	5	2
10.	Check whether the given polynomial $P(S) = S^5 + 7S^4 + 6S^3 + 9S^2 + 8S$ is Hurwitz or not	2	2	5	3
<b>Part-B (5 × 8 = 40 Marks)</b>					
11. a)	For the circuit shown in figure, find the values of all mesh currents using mesh analysis.	5	3	1	3
b)	Compare and contrast Tie-Set and Cut-Set in all respects.	3	2	1	2

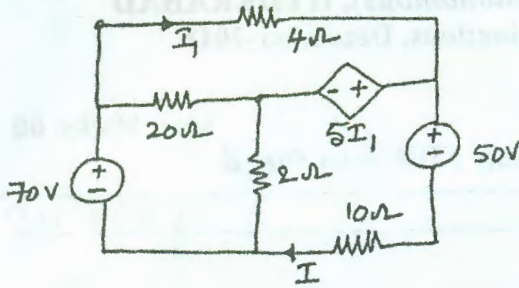a) Applying Super-position theorem, compute current I in the circuit shown in figure below:




5 3 2 4

b) Derive the condition of reciprocity for hybrid-Parameters.

3 2 2 3

13. a) The circuit shown in figure the switch 'S' is moved from position A to position B at  $t=0$ . Determine current through inductor  $i_L(t)$  for all  $t$ .

5 3 3 3

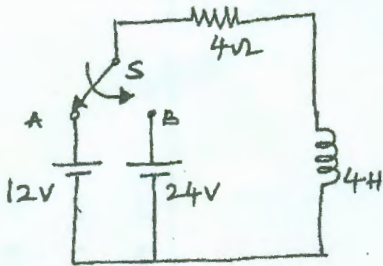


b) Describe the nature of roots for an RLC circuit along with neat sketches.

3 2 3 2

14. a) Analyze the given two-port network and evaluate the Z-parameters for the network shown below:

5 4 4 4

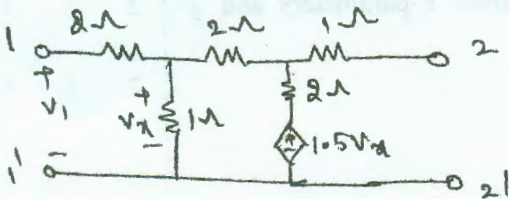

b) Formulate Transmission parameters in terms of Z-parameters.

3 2 4 3

15. a) Synthesize the impedance function  $Z(S) = \frac{2S^5 + 12S^3 + 16S}{S^4 + 4S^2 + 3}$  using Cauer form-I.


4 5 5 4

b) Synthesize the impedance function  $Z(S) = \frac{S+2}{(S+1)(S+3)}$  in Foster form-II.

4 5 5 4


16. a) For the circuit shown below:

4 3 1 3

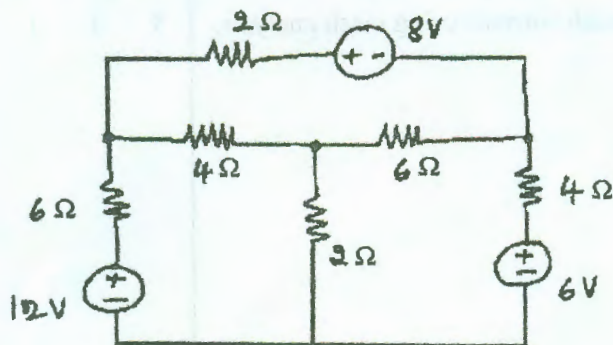



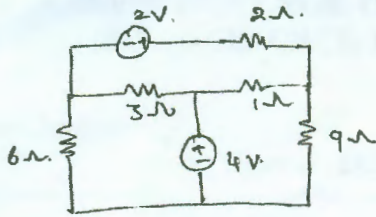b) By analyzing the circuit given, verify Tellegen's theorem.




4 2 2 3

17. Answer any *two* of the following:

a) Analyze the circuit given and evaluate the following:

- i)  $i_C(0+)$     ii)  $i_L(0+)$     iii)  $v_C(0+)$     iv)  $i_R(0+)$

4 4 3 3

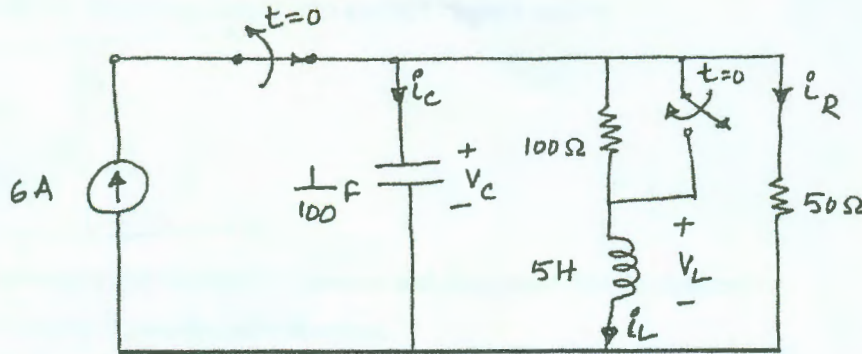

b) If the networks are interconnected in series-parallel manner, 'the overall h-parameters are the summation of individual h-parameters of the networks interconnected- Justify.

4 2 4 3

c) In a series RLC circuit, if the applied voltage is 10V, What is the voltage across the inductor if the resonance frequency is 1kHz and  $Q=10$ .

4 2 5 3

M: Marks; L: Bloom's Taxonomy Level; CO: Course Outcome; PO: Programme Outcome

S. No.	Criteria for questions	Percentage
1	Fundamental knowledge (Level-1 & 2)	53.75
2	Knowledge on application and analysis (Level-3 & 4)	36.25
3	*Critical thinking and ability to design (Level-5 & 6) (*wherever applicable)	10

CCCCCCCC