

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 13404 O3

**VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD**  
**B.E. (ECE) II Year I-Semester Old Examinations, May/June-2018**

**Electronic Materials & Devices**

Time: 3 hours

Max. Marks: 70

*Note: Answer ALL questions in Part-A and any FIVE from Part-B*

**Part-A (10 × 2 = 20 Marks)**

1. Define drift and diffusion currents in a semiconductor.
2. Explain the effect of rise in temperature on Voltage and current of a diode.
3. Calculate the value of capacitance to be used in a capacitor filter connected to a full wave rectifier operating at a frequency of 50Hz, if the ripple factor is 10% for a load of 500Ω.
4. State the principle of operation of a Tunnel diode.
5. Define  $\alpha$ ,  $\beta$  and  $\gamma$  for a BJT.
6. List the advantages of self-bias circuit.
7. Draw the h-parameter model for CE BJT amplifier.
8. What is intrinsic standoff ratio in a UJT?
9. Explain why FET is called a unipolar device.
10. A JFET has a drain current of 15mA. If  $I_{DSS}$  and  $V_p$  are 5mA and 5V respectively, find  $V_{GS}$ .

**Part-B (5 × 10 = 50 Marks)**

11. a) Define and derive an expression for diffusion capacitance of a diode. [6]  
b) The reverse saturation current of a Silicon PN diode is  $1\mu A$  at room temperature. Determine its ac resistance at 150mV forward bias. [4]
12. a) Draw and analyze a full wave rectifier with centre tapped transformer and find its PIV, ripple factor, TUF and efficiency. [5]  
b) Explain with energy band diagrams the operation and the V-I characteristics of a Tunnel Diode. [5]
13. a) Draw and explain the output characteristics of BJT in CB configuration. What are the three regions of operation? How can they be demarcated in the output characteristics? [6]  
b) Explain the current components of BJT and derive a relation between  $\alpha$  and  $\beta$ . [4]
14. a) Derive voltage gain and current gain for CE BJT amplifier using h-parameter model. [5]  
b) Explain the working of a DIAC and compare it with a TRIAC. [5]
15. a) Draw and explain the characteristics of a JFET. [5]  
b) Draw and explain the construction and operation of a depletion MOSFET. [5]
16. a) Write a short note on Zener voltage regulator and its limitations. [5]  
b) Write a short note on Light Emitting diode and state its applications. [5]
17. Answer any *two* of the following:  
a) Stability factor of BJT. [5]  
b) Write short notes on SCR. [5]  
c) List and explain FET applications. [5]