

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 22415

VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD
B.E. (Mech. Engg.) II Year II-Semester Main & Backlog Examinations, May-2017

Electrical Circuits and Machines

Time: 3 hours

Max. Marks: 70


Note: Answer ALL questions in Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

1. Define Ohm's law.
2. Define Thevenin's theorem.
3. Draw the Phasor diagram of a practical Transformer on no load.
4. What is the relationship between line and phase quantities in a 3-phase delta connected system?
5. What is the function of Commutator in a dc generator?
6. Why the generated EMF of a DC Motor is called back emf? Explain.
7. Draw the torque speed characteristics of an induction motor.
8. List out the methods of speed control of a 3 phase Induction motor.
9. What are the applications of stepper motor?
10. What are the applications of capacitor run motors?

Part-B (5 × 10 = 50 Marks)
(All bits carry equal marks)

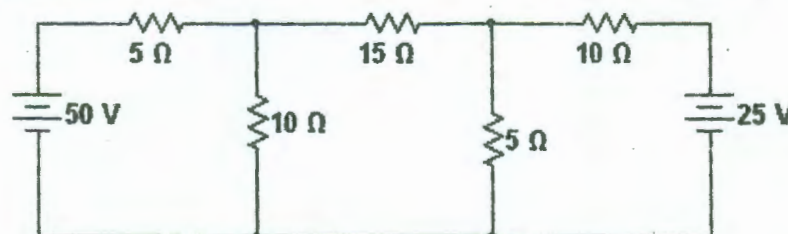11. a) Define i) r.m.s. value ii) average value iii) form factor of an alternating quantity.
b) Find the current flowing in each branch using loop current method.



12. a) A balanced 3 phase star connected load has an impedance of $5+j10$ ohm/phase. If a 3 phase, 415 V, 50 Hz supply is applied to the load, Find i) Phase current ii) Power absorbed by the load.
b) Draw the equivalent circuit of transformer and indicate all the parameters on it.
13. a) Derive the e.m.f. equation of d.c. generator.
b) A 200V, d.c. shunt generator has armature resistance of 0.1Ω and shunt field resistance of 100Ω . It supplies a load consisting of 50 lamps of each rated at 200 V, 100 W. Find the generated e.m.f.
14. a) How 3 Φ Induction motor is self-starting? Explain.
b) Explain the various starting methods of induction motor.

15. a) Explain the construction and principle of operation of capacitor start single phase induction motor.

b) With a neat sketch explain the basic features of a permanent magnet stepper motor.

16. a) A resistance of 20Ω , inductance of 50mH and a capacitance of $20 \mu\text{F}$ are connected in series and fed from a 250V , 50 Hz single phase a.c. supply.

Find i) impedance ii) current iii) power consumed and iv) power factor.

b) A 10kVA , $2500/250 \text{ V}$ single phase transformer gave the following test results:

O C Test: 250 V 0.8 A 50W

S.C Test: 60 V 3A 45 W

Calculate the efficiency at full load, unity power factor.

17. Write short notes on any *two* of the following:

a) Speed control of d.c series motor.

b) Rotating magnetic field of $3 \Phi \text{ IM}$.

c) Applications of variable frequency drives.

