

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 15401 S

VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD
B.E. (ECE: CBCS) V-Semester Supplementary Examinations, May-2019

Integrated Circuits and Applications

Time: 3 hours

Max. Marks: 70

Note: Answer ALL questions in Part-A and any FIVE from Part-B


Part-A (10 × 2 = 20 Marks)

1. Define slew rate and write its significance.
2. State the requirements of a good instrumentation amplifier?
3. Draw the circuit diagram of Schmitt trigger using 555 Timer.
4. Design a second order Butterworth low pass filter for cutoff frequency of 1.5KHz.
5. Find the resolution of 8-bit DAC for full scale output voltage of 10V.
6. Draw the circuit diagram of 2-bit parallel type ADC.
7. List salient characteristics of digital integrated circuits.
8. What is the drawback of open collector configuration? How it eliminated in Tristate logic?
9. Design a mod-10 Johnson counter.
10. Write the differences between static RAM and Dynamic RAM.

Part-B (5 × 10 = 50 Marks)

- 11.a) Describe the operation of ideal integrator with the help of circuit diagram and give its applications. [6]
b) Design an op-amp based application circuit to get an output voltage $V_0 = 5V_1 - 2V_2 - 3V_3$ [4]
- 12.a) Explain the functional diagram of 8038 and also derive the expression for frequency of oscillation. [6]
b) Design a PLL circuit using IC565 for a free running frequency of 400KHz and capture range of ± 10 KHz with a supply voltage of $\pm 6V$. [4]
- 13.a) Describe the working of Dual Slope ADC with a neat circuit diagram. [6]
b) For 4-bit Dual slope ADC, consider $R=100K\Omega$, $C=1\mu F$, clock frequency is 10 KHz, $V_{ref} = -6V$ and $V_{in} = 3V$. Determine the output count and conversion time after the conversion is completed [4]
- 14.a) Draw the circuit diagram of three input CMOS NAND gate and explain its operation. [5]
b) Design a BCD adder using IC 7483. [5]
- 15.a) Describe the principle of operation of parallel in serial out shift register and give its applications. [5]
b) Implement the logic function $F_1(a,b,c) = \sum(1,3,5,7)$ and $F_2(a,b,c) = \sum(0,2,3,7)$ using PAL and PLA [5]

 - 16.a) Design a 5V voltage regulator using IC723 for load current of 600mA under short circuit condition. [5]
- b) Design a Narrow BSF to meet the following specifications: $f_c = 2\text{KHz}$, $Q=20$ and $A_F=10$. [5]
- 17. Answer any *two* of the following:
 - a) Determine the frequency at the output of the following circuit. [5]



- b) Explain the working of 3-bit R-2R ladder type DAC. [5]
- c) Compare the key characteristics of TTL, ECL and CMOS logic families. [5]
