

Hall Ticket Number:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Code No. : 22716

VASAVI COLLEGE OF ENGINEERING (Autonomous), HYDERABAD
M.E. (EEE: CBCS) II-Semester Main Examinations, June-2018
(Power Systems & Power Electronics)

Programmable Logic Controllers and their Applications

Time: 3 hours

Max. Marks: 60

Note: Answer ALL questions in Part-A and any FIVE from Part-B

Part-A (10 × 2 = 20 Marks)

1. Name any 2 digital and 2 analog input devices connected to PLC.
2. List the important units of a PLC.
3. There are 2 machines, each with its own start-stop buttons. Only one may run at a time. Construct a circuit appropriate interlocking.
4. What is the function of EX-OR Gate?
5. Draw and discuss the Timer ON delay function.
6. Define the PLC Multiplication function.
7. Illustrate the SKIP function of a PLC.
8. Define the concepts of Matrix function.
9. Differentiate between Discrete and Analog Operation of a PLC.
10. Illustrate the procedure of Analog Signal Processing in PLC.

Part-B (5 × 8 = 40 Marks)

11. a) List out 4 advantages and disadvantages of PLC. [4]
b) Explain the working of a PLC Output Module Layout, with a neat block diagram. [4]
12. a) With neat diagram explain PLC Scanning in detail. [4]
b) Implement 4x1 multiplexer in Ladder diagram. [4]
13. a) Describe the UP-Down Counter. [3]
b) When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. [5]
14. a) What is the function used for moving a large block of PLC data? Explain in detail. [3]
b) Explain basic Two-axis Robot with PLC sequencer control. [5]
15. a) Describe PID function of PLC in detail. [4]
b) Explain the PLC Analog Output application examples. [4]
 - Analog In/Discrete out.
 - BCD in/BCD or Analog output.
16. a) Illustrate the PLC Power Supply Module. [4]
b) Explain with Ladder diagram, the forward and reverse direction control of a motor with a Fail-Safe operation. [4]
17. Answer any *two* of the following:
 - a) List and define the six basic COMPARE functions. [4]
 - b) Describe working of a jump with nonreturn instruction. [4]
 - c) Explain different methods of PID tuning. [4]